

Assignment 1

February 4, 2023 1:17 AM

ENGI-1500 Physics-2

Winter-2023

Assignment-1

1 Assignment Prepared By (Individual Work)

Assignment Due: February 7, 2023 – 11:59 pm

Please submit on Blackboard / email

Name: Michael McCorkell
Student ID: N01500049

Humber College Institute of Technology and Advanced Learning

Textbook: Serway, Raymond A., and John W. Jewett. Physics for scientists and engineers. 10th Edition. Cengage learning, 2018.



ENGI-1500 Physics-2

Winter-2023

2 Questions


Q1 [Textbook 22.33] [20 pts]

T A charged cork ball of mass 1.00 g is suspended on a light string in the presence of a uniform electric field as shown in [Figure P22.33](#).

When $\vec{E} = (3.00\hat{i} + 5.00\hat{j}) \times 10^5 \text{ N/C}$, the ball is in equilibrium at $\theta = 37.0^\circ$. Find

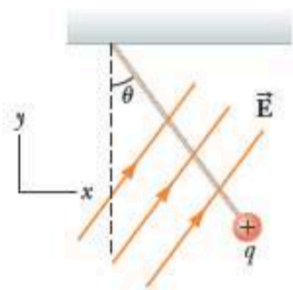- (a) the charge on the ball and
- (b) the tension in the string.





$$\sum F = 1 + qE \cdot 19$$

$$E_x = 3.00 \hat{i} \cdot 10^5 \text{ N/C}$$

$$E_y = 5.00 \hat{j} \cdot 10^5 \text{ N/C}$$

Applying Newton's second law or the first condition for equilibrium in the x & y directions,

$$\sum F_x = qE_x - T \sin 37^\circ = 0 \quad [eq1]$$

$$\sum F_y = qE_y + T \cos 37^\circ - mg = 0 \quad [eq2]$$

Figure [22.33]: A charged ball suspended on a string.

a) Solve for T from eq1

$$T = \frac{qE_x}{\sin 37^\circ}$$

$$q = \frac{mg}{E_y + \frac{E_x}{\tan 37^\circ}}$$

$$= \frac{(1.00 \cdot 10^{-2} \text{ kg})(9.80 \text{ m/s}^2)}{5.10 \text{ N/C} + \left(\frac{3.00 \text{ N/C}}{\tan 37^\circ}\right)}$$

$$q = 1.09 \cdot 10^{-8} \text{ C}$$


$$b) \quad T = \frac{qE_x}{\sin 37^\circ}$$

$$= \frac{(1.09 \cdot 10^{-8} \text{ C})(3.10^5 \text{ N/C})}{\sin 37^\circ}$$

$$T = 5.44 \cdot 10^{-3} \text{ N}$$

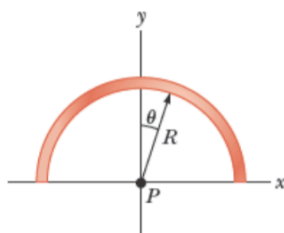Q2 [Textbook 23.41] [20 pts]

A line of positive charge is formed into a semicircle of radius $R = 60.0 \text{ cm}$ as shown in [Figure P23.41](#). The charge per unit length along the semicircle is given by the expression $\lambda = \lambda_0 \cos \theta$. The total charge on the semicircle is $12.0 \mu\text{C}$. Calculate the total force on a charge of $3.00 \mu\text{C}$ placed at the center of curvature P .



$$\lambda_0 = \frac{Q}{2R}$$

$$= \frac{12 \cdot 10^{-6}}{2(0.6)}$$

$$= 1 \cdot 10^{-5} \text{ C}$$

Figure [23.41]: Electric force due to continuous charge distribution.

$$F_e = qE$$

$$= -\frac{\pi K_e \lambda_0 q}{2R}$$

$$F_e = - \frac{\pi (8.88 \times 10^{-12}) (1 \times 10^{-5}) (3 \times 10^{-4})}{2(0.6)}$$

$$= -706 \times 10^{-3} \text{ N}$$


(-) Indicates that the total force is directed in the negative direction

$$F_e = - (706 \times 10^{-3} \text{ N}) \text{ J}$$

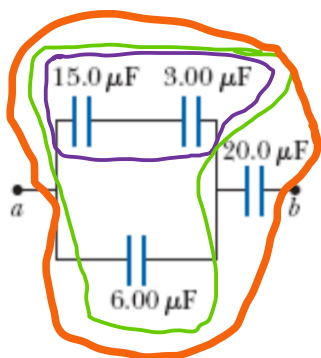Q3 [Textbook 25.11] [20 pts]

Four capacitors are connected as shown in Figure P25.11.

- Find the equivalent capacitance between points *a* and *b*.
- Calculate the charge on each capacitor, taking $\Delta V_{ab} = 15.0 \text{ V}$.



a) $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00}$
 $\frac{1}{C_s} = 0.4$
 $C_s = 2.50 \mu\text{F}$

$C_p = 2.50 \mu\text{F} + 6.00 \mu\text{F}$
 $C_p = 8.50 \mu\text{F}$

$C_{eq} = \frac{1}{\left(\frac{1}{8.50} + \frac{1}{20.0}\right)}$

$C_q = \frac{1}{\frac{1}{8.50}}$

$C_{eq} = 5.96 \mu\text{F}$

Figure [25.11]: Capacitor combination.

b)

$$Q = C \Delta V = (5.96 \mu\text{F})(15\text{V})$$

$$= 89.5 \mu\text{C} \text{ on } 20 \mu\text{F}$$

$$\Delta V = \frac{Q}{C} = \frac{89.5 \mu\text{C}}{20.0 \mu\text{F}} = 4.47\text{V}$$

$$15\text{V} - 4.47\text{V} = 10.53\text{V}$$

$$Q = C \Delta V = (6 \mu\text{F})(10.53\text{V})$$

$$= 63.2 \mu\text{C} \text{ on } 6 \mu\text{F}$$

$$89.5 - 63.2 = 26.3 \mu\text{C} \text{ on } 15 \mu\text{F} \& 3 \mu\text{F}$$

Q4 [Textbook 26.30] [20 pts]

An 11.0-W energy-efficient fluorescent lightbulb is designed to produce the same illumination as a conventional 40.0-W incandescent lightbulb. Assuming a cost of \$0.110/kWh for energy from the electric company, how much money does the user of the energy-efficient bulb save during 100 h of use?

Bulb 1 = Power $\rightarrow 11.0W$
 Bulb 2 = Power $\rightarrow 40W$
 Cost / energy = \$0.110/kWh
 $t = 100$ hours

$$E = P \cdot t$$



$$E_{B1} = \frac{11 \cdot 100}{1000} = 1.1 \text{ KWH}$$

$$E_{B2} = \frac{40 \cdot 100}{1000} = 4 \text{ KWH}$$

$$(4 - 1.1) \cdot 0.110 = 2.9 \cdot 0.110 = 0.319$$

total money saved would be \$0.319

Q5 [Textbook 27.22] [20 pts]

  For the circuit shown in Figure P27.22, we wish to find the currents I_1 , I_2 , and I_3 . Use Kirchhoff's rules to obtain equations for

- the upper loop,
- the lower loop, and
- the junction on the left side. In each case, suppress units for clarity and simplify, combining the terms.

$$\begin{aligned}
 \text{a)} \quad & \begin{bmatrix} -(11\Omega)I_1 + 12V - (7\Omega)I_2 \\ -(6\Omega)I_1 + 18V - (8\Omega)I_1 \end{bmatrix} = 0 \\
 & (13\Omega)I_1 + (18\Omega)I_2 = 30V \quad \text{①} \\
 \text{b)} \quad & \begin{bmatrix} -(6\Omega)I_1 + 18V + (7\Omega)I_2 \\ -12V + (11\Omega)I_2 \end{bmatrix} = 0 \\
 & (18\Omega)I_2 - (6\Omega)I_1 = -24V \quad \text{②}
 \end{aligned}$$

(d) Solve the junction equation for I_3 .

(e) Using the equation found in part (d), eliminate I_3 from the equation found in part (b).

(f) Solve the equations found in parts (a) and (e) simultaneously for the two unknowns I_1 and I_2 .

(g) Substitute the answers found in part (f) into the junction equation found in part (d), solving for I_3 .

(h) What is the significance of the negative answer for I_3 ?

c) $I_1 - I_2 - I_3 = 0$ ⑤

d) $I_3 = I_1 - I_2$

e) $(18\Omega)I_1 - (5\Omega)(I_1 - I_2) = -24V$

$(18\Omega)I_1 - (5\Omega)I_1 + (5\Omega)I_2 = -24V$ ④

$(5\Omega)I_1 - (23\Omega)I_2 = 24V$

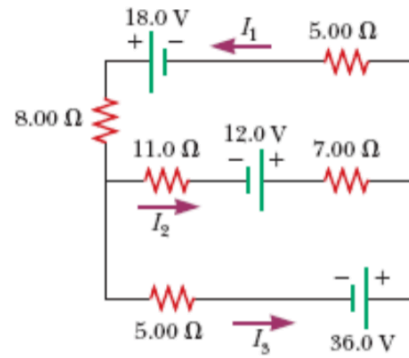


Figure [27.22]: Circuit diagram.

g) $I_3 = I_1 - I_2$
 $I_3 = 2.88 - (-0.416)$
 $I_3 = 3.29 A$

f) $(5\Omega)I_1 - (23\Omega)I_2 = 24V$

$I_1 = \frac{24V + (23\Omega)I_2}{5\Omega}$ ⑤

$(18\Omega)I_1 + (18\Omega)I_2 = 30V$

$(18\Omega)\left(\frac{24V + (23\Omega)I_2}{5\Omega}\right) + (18\Omega)I_2 = 30V$

$13\Omega((24V + 23\Omega)I_2) + (5\Omega)(18\Omega)I_2 = 30V \cdot 5\Omega$

$312\Omega V + (299\Omega^2)I_2 + (90\Omega^2)I_2 = 150\Omega V$

$(389\Omega^2)I_2 = -162\Omega V$

$I_2 = \frac{-162\Omega V}{(389\Omega^2)}$

$I_2 = -0.416 A$

$I_1 = \frac{24V + (23\Omega)(-0.416A)}{5\Omega}$

$I_1 = 2.88 A$

h) It means that the current flows in the opposite direction.