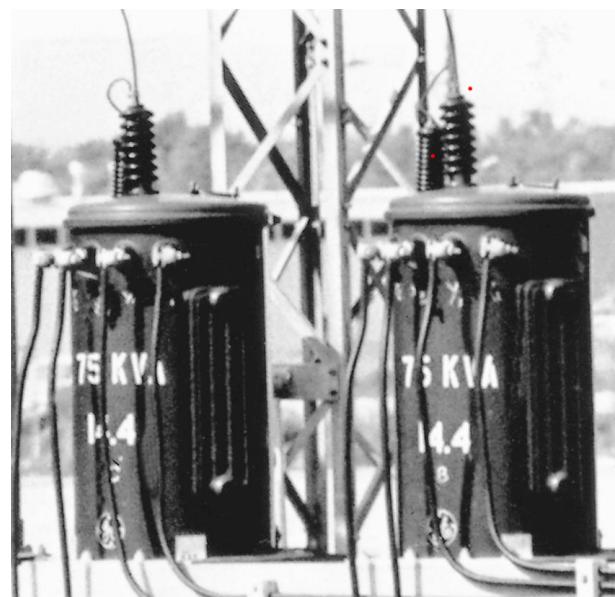
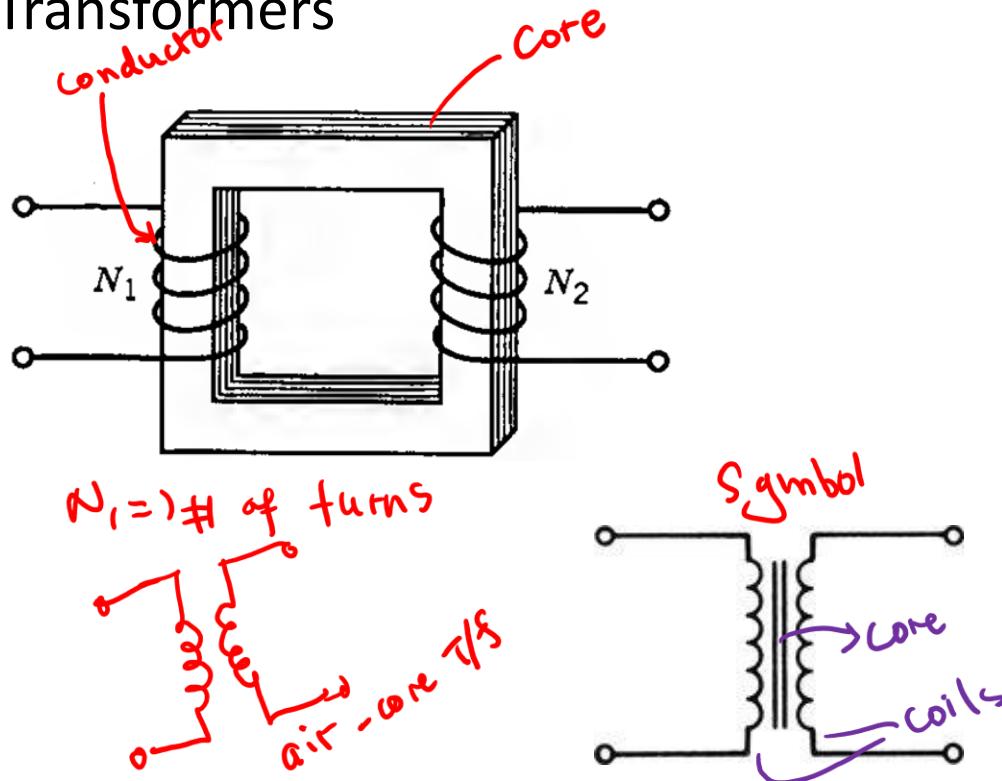

Transformers

Introduction

machine



- A transformer is a static machine (no rotating parts)
- A transformer consists of two or more windings coupled by a mutual magnetic field
good magnetic material
- Ferromagnetic cores are used to provide high magnetic coupling and high flux densities
- Iron Core (High Power) Vs Air core (low power electronic circuits)

Transformers




Introduction

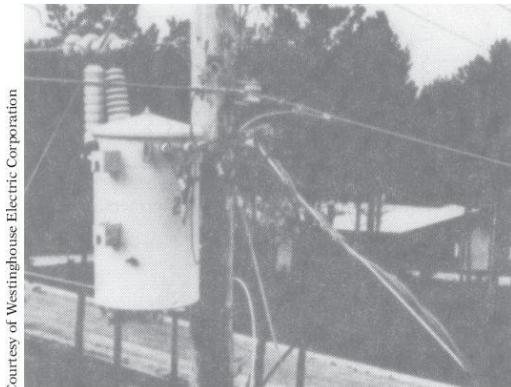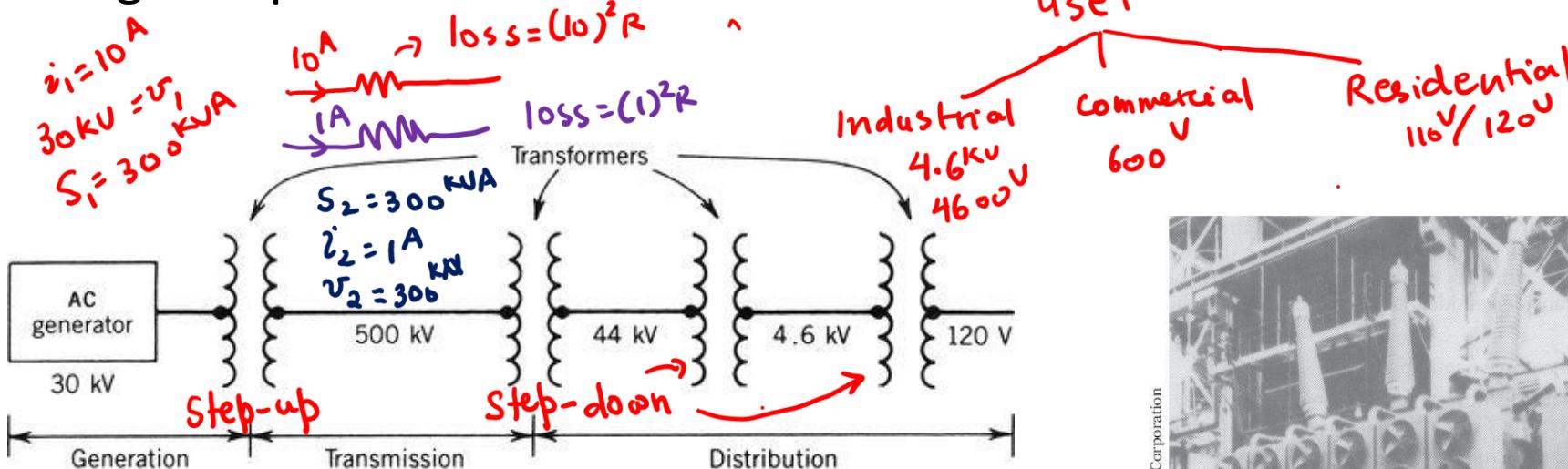- Transformers have widespread use
- The primary function of a transformer is to change the voltage level
- Transformers are used to step up and step down voltage at various stages of power transmission



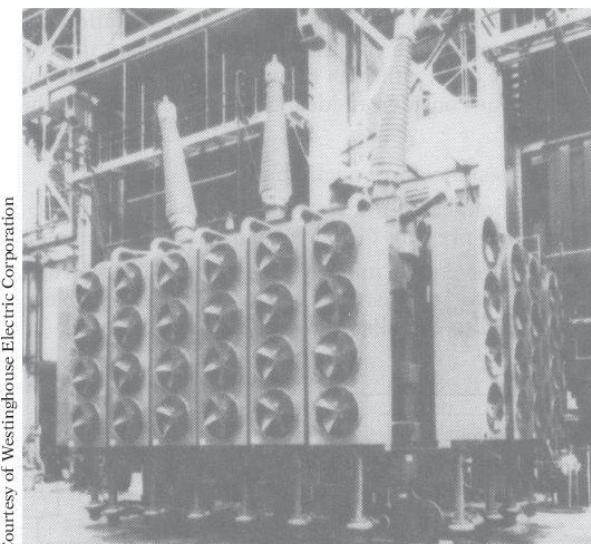
Distribution Transformer to step down the voltage from 4.6 kV to 120 V



Power Transformer to step up the voltage from 24 kV to 345 kV

Introduction

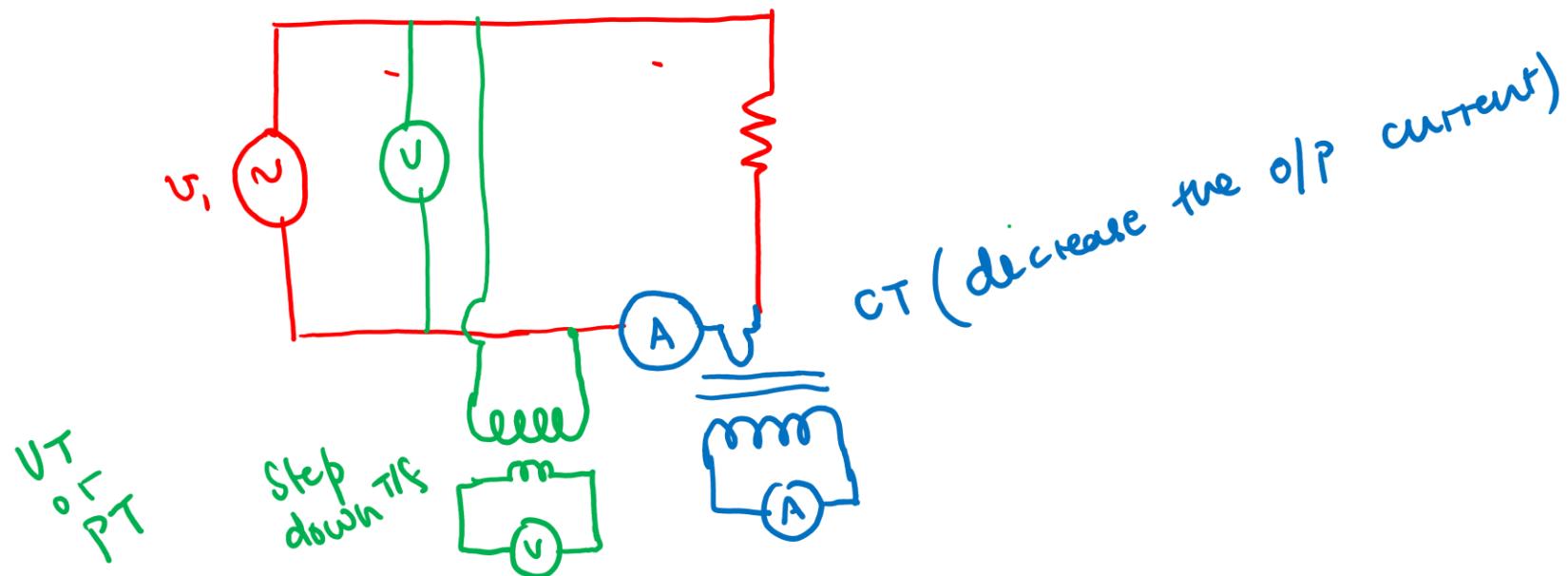
- Transformers are also used in low power applications
- Low power electronic or control circuits to isolate one circuit from the other or to ⁽³⁾ match the impedance of a source with its load for maximum power transfer
- ⁽⁴⁾ Transformers are also used for voltage and current measurements
 - Instrument Transformers




Ideal Transformer

magnetic field $\leftarrow \frac{\Phi}{B} H$

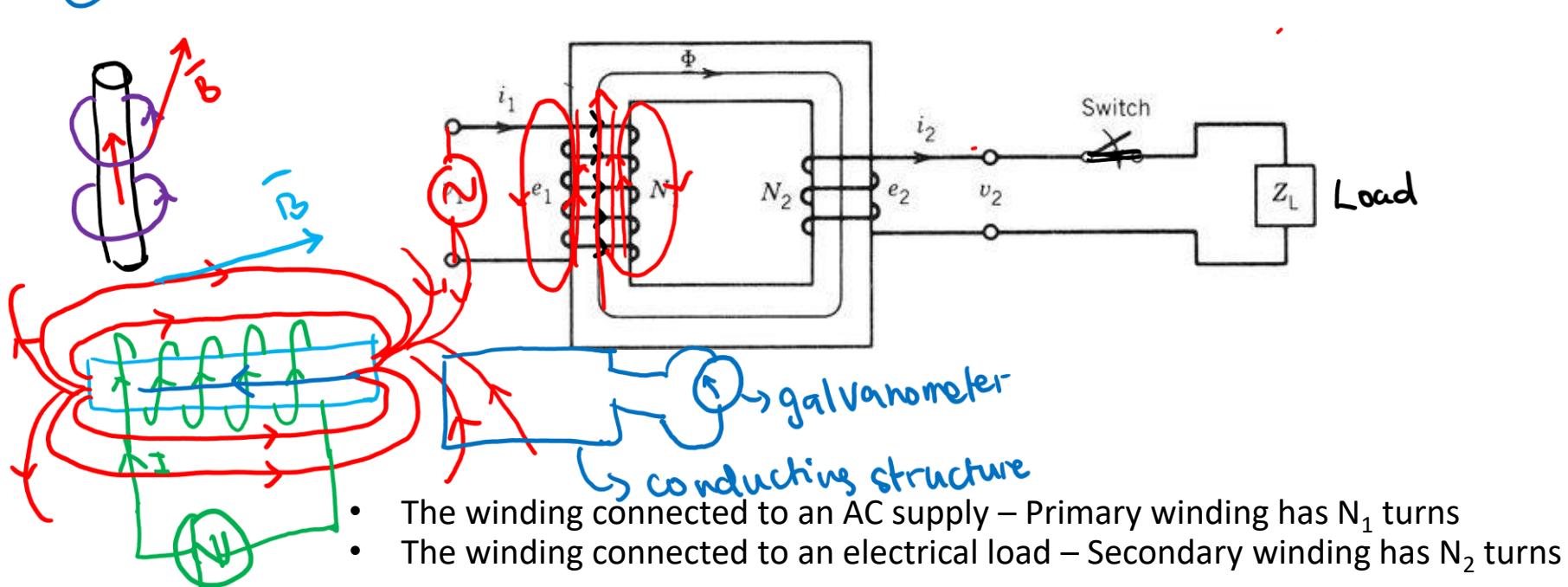1. The winding resistance is negligible
2. All fluxes are confined to the core and link both windings; that is, no leakage fluxes are present
3. Permeability of the core is infinite. Therefore, the exciting current required to establish flux in the core is negligible.
4. No eddy current and hysteresis losses



Ideal Transformer

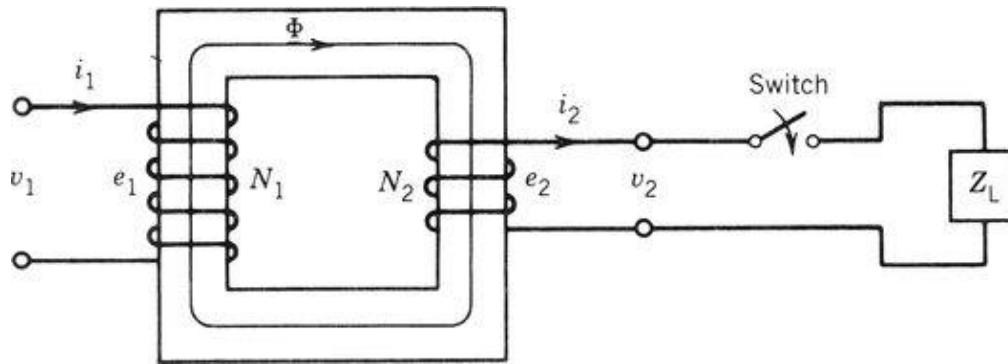

Faraday's law:

$$v_1 = e_1 = N_1 \frac{d\Phi}{dt}$$

$$v_2 = e_2 = N_2 \frac{d\Phi}{dt}$$

$$\frac{v_1}{v_2} = \frac{N_1 \cancel{\frac{d\Phi}{dt}}}{N_2 \cancel{\frac{d\Phi}{dt}}} = \frac{N_1}{N_2}$$

$$\boxed{\frac{v_1}{v_2} = \frac{N_1}{N_2} = a}$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

$$\begin{matrix} N_1 > N_2 \\ 10 & 5 \end{matrix}$$

$$\frac{v_1}{v_2} = \frac{10}{5}$$

$$v_1 = \frac{10}{5} v_2$$

$v_1 > v_2$
Step-down T/f

$$\begin{matrix} N_1 < N_2 \\ 5 & 10 \end{matrix}$$


$$v_1 = \frac{5}{10} v_2 = \frac{1}{2} v_2$$

$$v_2 > v_1$$

Step-up T/f.

a turns ratio

Ideal Transformer

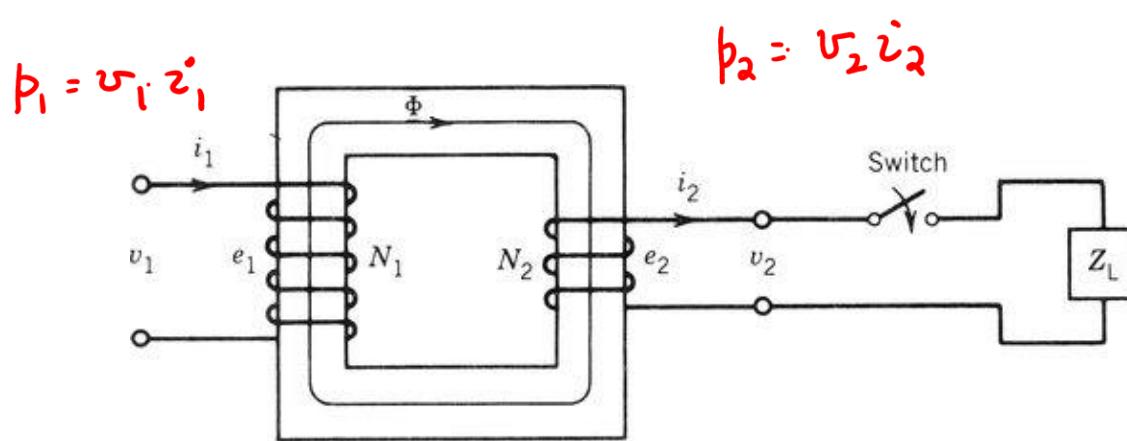

No power losses:

$$\oint B \cdot d\ell = \Phi$$



$$\frac{v_1 i_1}{v_2 i_2} = \frac{v_2 i_2}{v_1 i_1}$$

$$\frac{N_1}{N_2} = \frac{v_1}{v_2} = \frac{i_2}{i_1}$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} = \frac{i_2}{i_1}$$

a turns ratio

Ideal Transformer

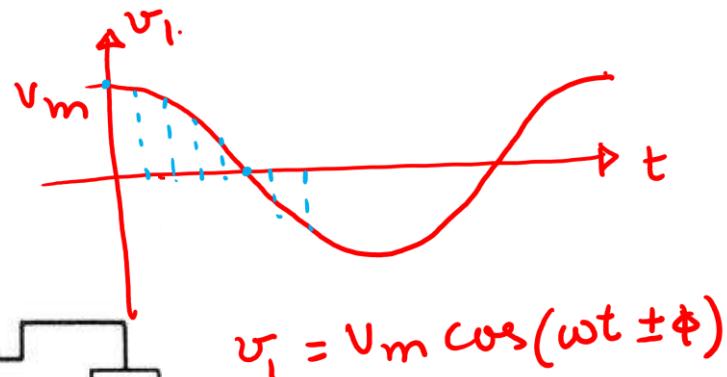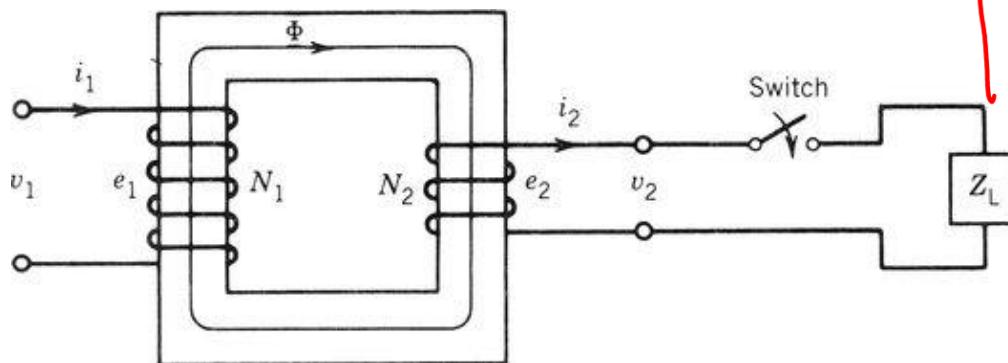

For Sinusoidal supply voltage v_1 , in terms of RMS values of the quantities

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$V_1 I_1 = V_2 I_2$$

Ideal Transformer; Example

$$\omega = 377 \text{ rad/sec}$$

$\omega \rightarrow \text{angular freq.}$
 $\omega = 2\pi f$
 $f = \frac{377}{2\pi} = 60 \text{ Hz}$

If $v_1 = 120\sqrt{2} \cos(377t)$, $i_2 = 10\sqrt{2} \cos\left(377t - \frac{\pi}{6}\right)$,
 calculate v_2 and i_1

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$


$$v_2 = \frac{N_2}{N_1} v_1 = \frac{20}{100} [120\sqrt{2} \cos(377t)]$$

$$v_2 = 24\sqrt{2} \cos(377t)$$




$$\frac{i_2}{i_1} = \frac{N_1}{N_2}$$

$$i_1 = \frac{N_2}{N_1} i_2 = \frac{20}{100} [10\sqrt{2} \cos(377t - \frac{\pi}{6})]$$

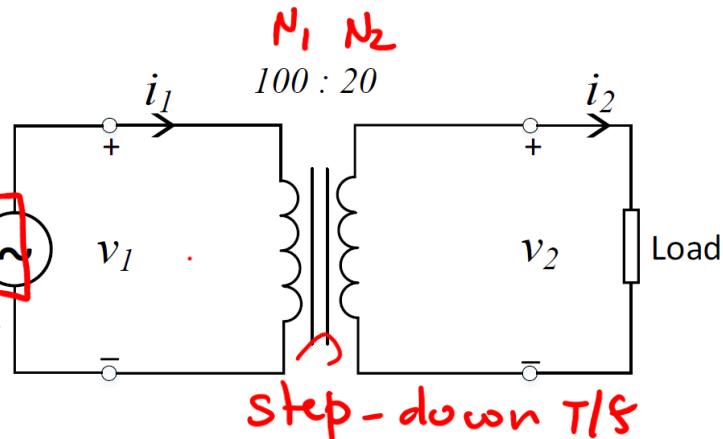
$$i_1 = 2\sqrt{2} \cos(377t - \frac{\pi}{6})$$



Ideal Transformer: Polarity dots

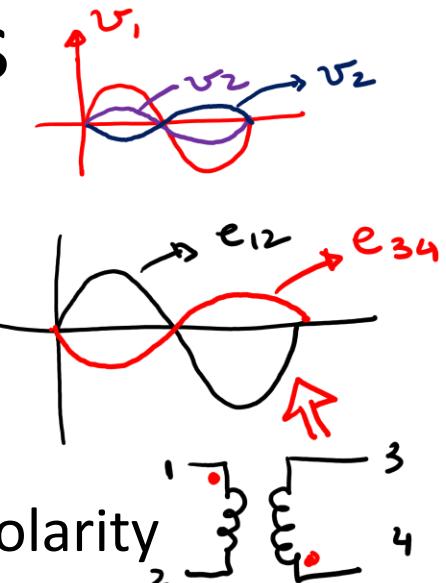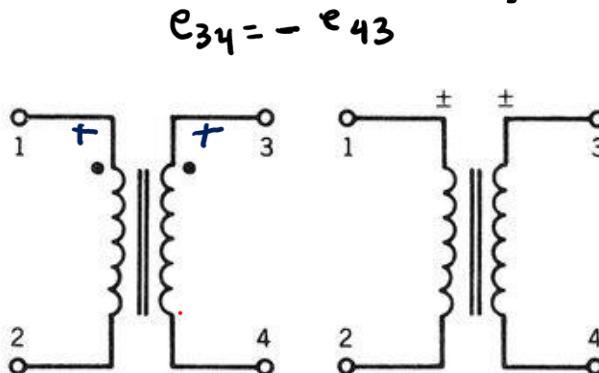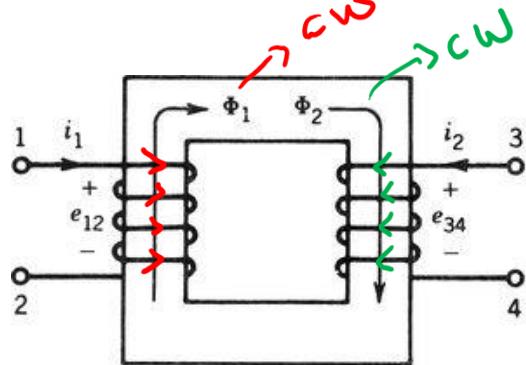


- Windings are marked to indicate terminals of like polarity
- Terminals 1 and 3 are identical because currents entering these terminals produce fluxes in the same direction in the core that forms a common path
- If the two windings are linked by a common time varying flux, voltages will be induced in these windings such that at a particular instant the potential of terminal 1 is positive w.r.t terminal 2, then at the same instant the potential of terminal 3 will be positive w.r.t terminal 4. The induced voltage e_{12} and e_{34} are in phase

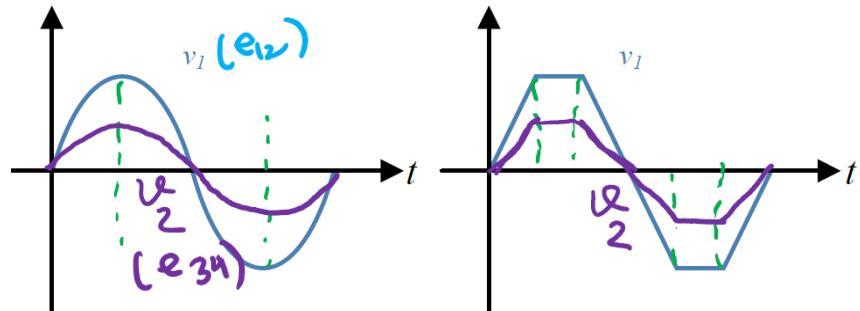


Ideal Transformer: Impedance Transfer

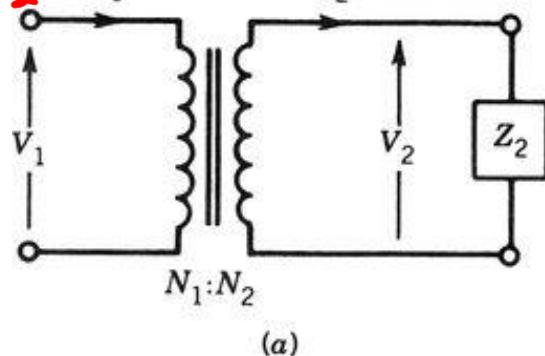$V_1, I_1 \rightarrow$ primary side quantities
 $V_2, I_2, Z_2 \rightarrow$ secondary side quantities



(a)

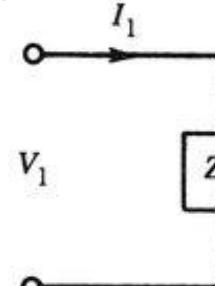

(b)

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = a$$

$\boxed{N_1, N_2, Z_2}$

$$a = \frac{I_2}{I_1}$$

$$\left| z'_1 = \boxed{z_2} = \frac{V_2}{I_2} = \frac{V_1/a}{I_2/a} = \frac{V_1}{a^2 I_1} = \frac{1}{a^2} \left(\frac{V_1}{I_1} \right) \right.$$

$$z'_1 = \frac{1}{a^2} z_1$$


transfer secondary side impedance Z_2 to the primary side

$$z'_2 = \boxed{z_1} = \frac{V_1}{I_1} = \frac{a V_2}{I_2/a} = \frac{a^2 V_2}{I_2} = a^2 \left(\frac{V_2}{I_2} \right) = a^2 Z_2$$

transferred / reflected /
 \uparrow reflected impedance
 to the primary side

$$Z'_2 = a^2 Z_2$$

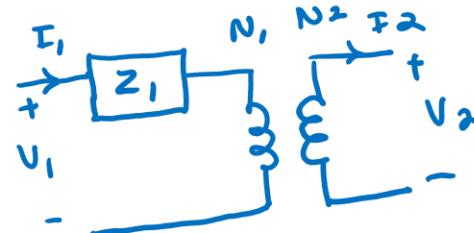An impedance Z_2 connected in the secondary will appear as an impedance Z'_2 on the primary side





$$Z'_1 = \frac{1}{a^2} Z_1$$

An impedance Z_1 can be transferred from primary side to the secondary side as Z'_1

Ideal Transformer: Impedance Transfer: Example

A speaker of $9\ \Omega$, resistive impedance is connected to supply of 10 V with internal resistive impedance of $1\ \Omega$.

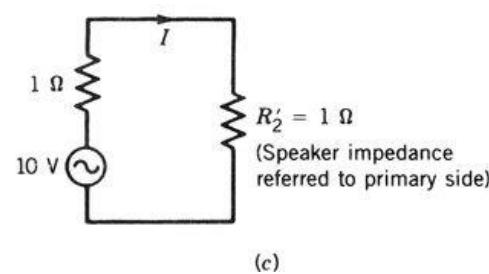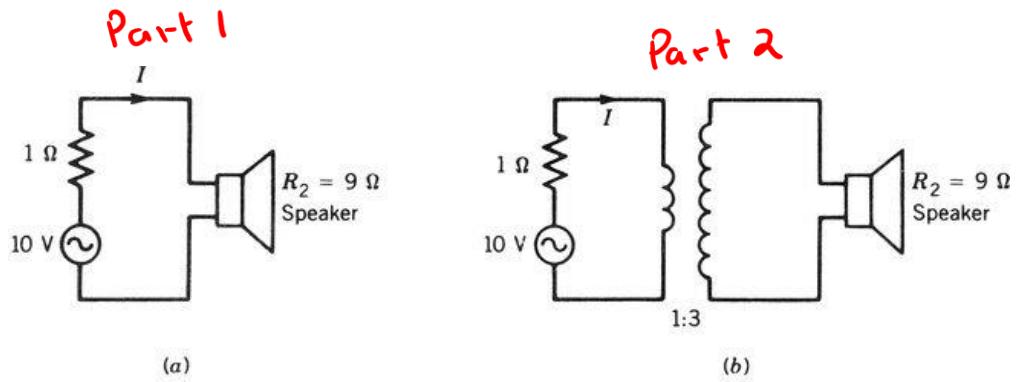1. Calculate the power absorbed by the speaker
2. To maximize the power transfer to the speaker, a transformer of $1:3$ turns ratio is used between source and speaker. Determine the power taken by the speaker






$$R'_2 = a^2 R_2$$

① $P_{\text{speaker}} = P_{R_2} = V_{R_2} I_{R_2} = (I_{R_2})^2 R_2 = (I^2) R_2 \quad 10\text{ V}$

$$I = \frac{10\text{ V}}{(1+9)} = 1\text{ A}$$

$$P_{\text{speaker}} = 1^2 \times 9 = 9\text{ W}$$

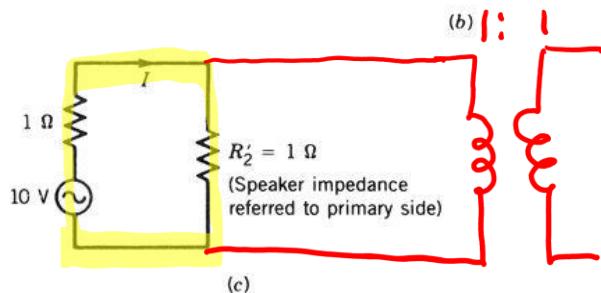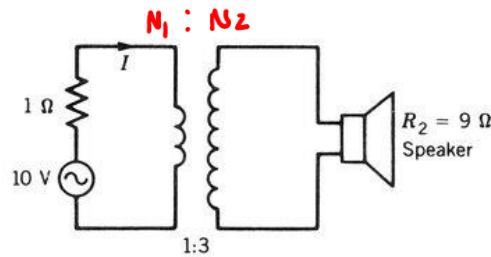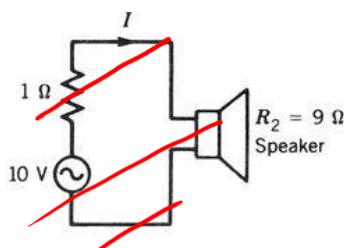Ideal Transformer: Impedance Transfer: Example



$$R'_2 = a^2 R_2$$


$$a = \frac{N_1}{N_2} = \frac{1}{3}$$

$$R'_2 = \left(\frac{1}{3}\right)^2 \times 9 = \frac{1}{9} \times 9 = 1 \Omega$$



$$I = \frac{10}{1+1} = \frac{10}{2} = 5 \text{ A}$$

$$P_{R'_2} = P_{\text{Speaker}} = (I)^2 \times 1 = 5^2 \times 1 = 25 \text{ W}$$

Practical Transformer

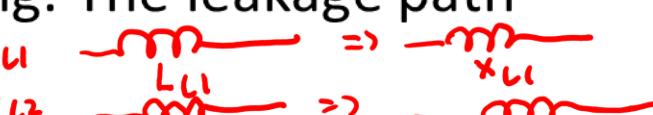
1. The winding has resistance – wires have resistance (R_1 and R_2)
2. All fluxes are essentially confined to the core. However, a small amount of the flux known as leakage flux, φ_l links only one winding and does not link the other winding. The leakage path is in air. 
3. Permeability of the core is finite. A magnetizing current I_m is required to establish flux in the core. The core losses are represented by R_c

$$I_{\varphi_1} = I_{m1} + I_{c1}$$

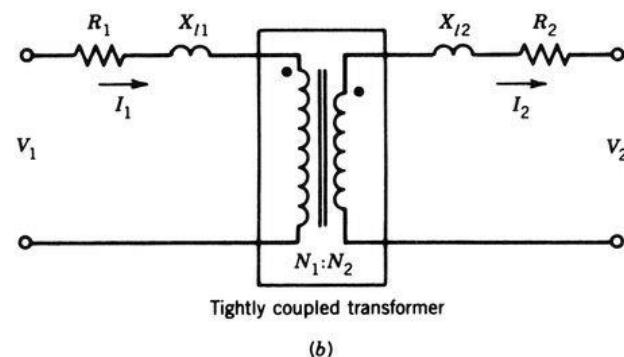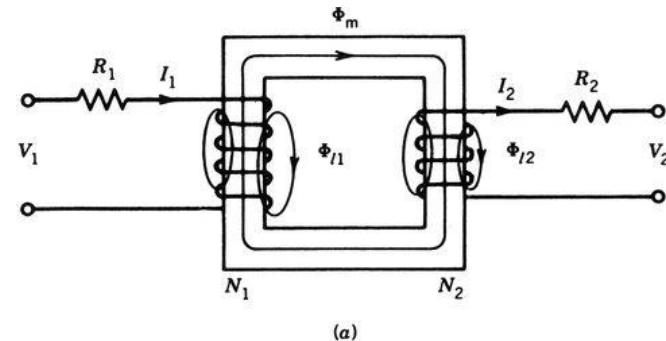

$x = 2\pi f L$

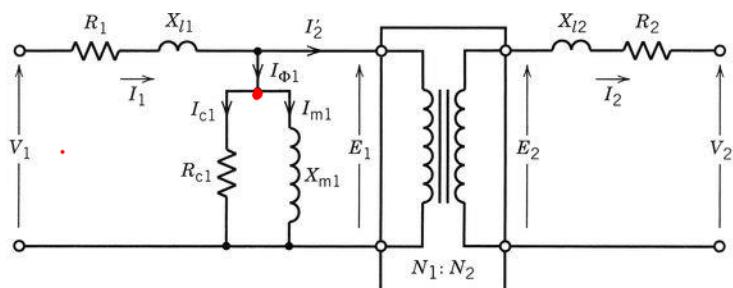\rightarrow  $x_m \rightarrow$ magnetizing reactance



Practical Transformer eq. circuit

Practical Transformer: Equivalent circuit

The ideal transformer can be moved to the right or to the left by referring all quantities to the primary or secondary side, respectively.

diagram (c): ideal transformer moved to the right

diagram (d): ideal transformer is not shown, all quantities referred to one side



$$\alpha = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

R_2 → secondary resistance

R'_2 → secondary resistance reflected to primary side


$$R'_2 = \alpha^2 R_2$$

$$X'_{l2} = \alpha^2 X_{l2}$$

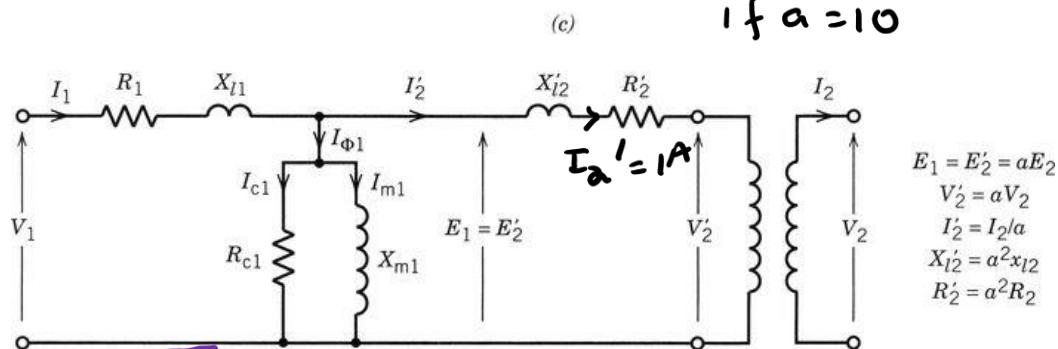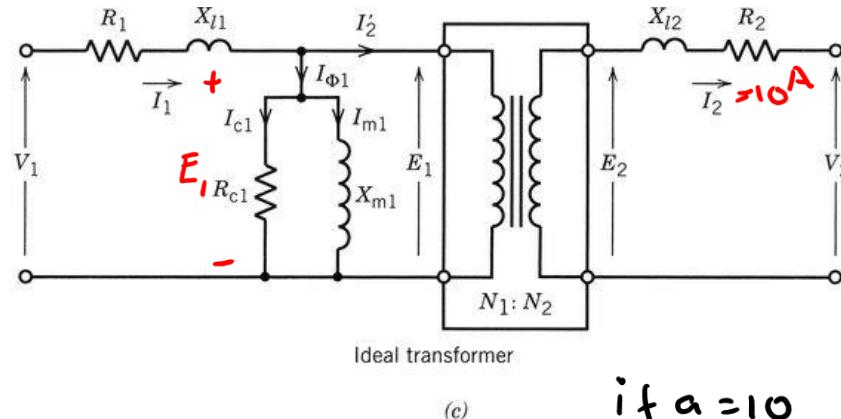

$$I'_2 = I_1 = \frac{I_2}{\alpha}$$
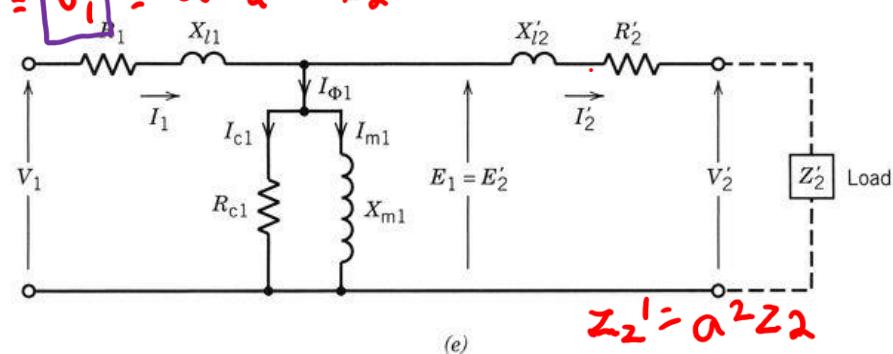
$$V'_1 = V_1 = \alpha V_2 \quad E'_2 = \alpha E_2$$





Practical Transformer: Approximate Equivalent circuit

The voltage drop $I_1 R_1$ and $I_1 X_{L1}$ are normally small and $V_1 \approx E_1$, then the shunt branch can be moved to the supply terminals diagram (a) diagram (b) and (c), as the exciting current I_ϕ is small, the excitation (shunt) branch can be completely neglected

$$I_1 = I_{eq1} + I_{a'}$$


$$I_{eq1} \rightarrow \text{small}$$

$$I_{eq1} \approx 0$$

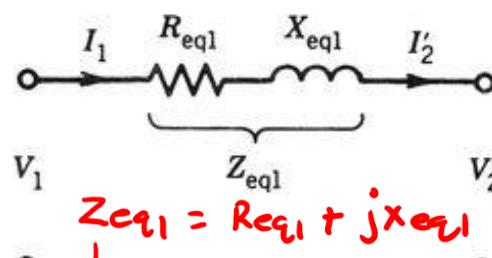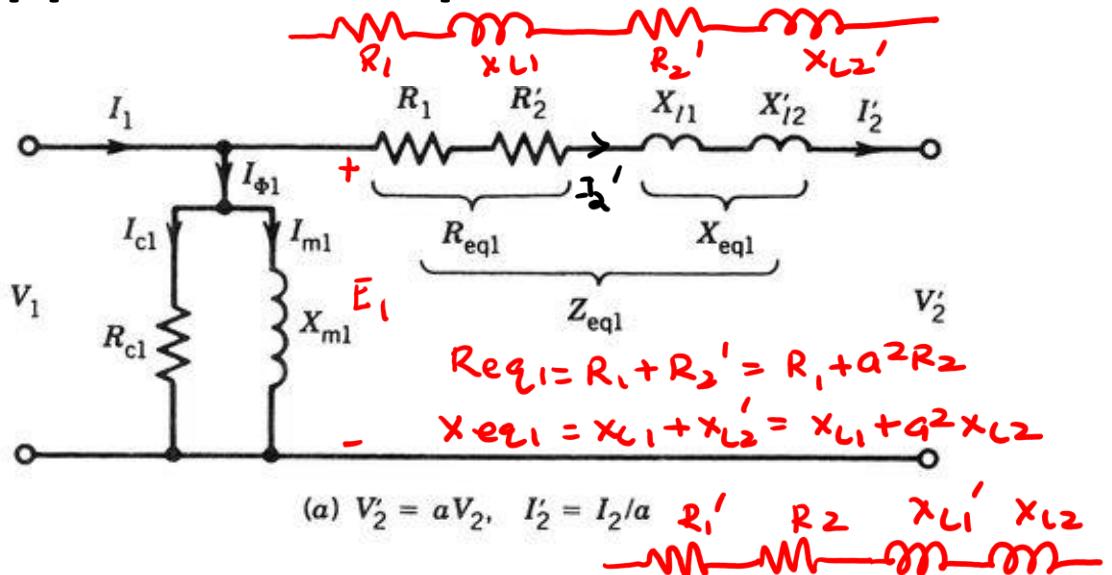

$$Z_{eq1} = R_{eq1} + jX_{eq1}$$

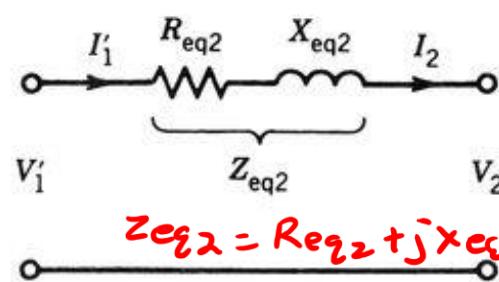(b) Referred to side 1, $Z_{eq1} = R_{eq1} + jX_{eq1}$



$$Z_{eq2} = R_{eq2} + jX_{eq2}$$

(c) Referred to side 2, $Z_{eq2} = R_{eq2} + jX_{eq2}$

complex quantity

$$R_{eq2} = \frac{R_{eq1}}{a^2} = R_2 + R_1' = R_2 + \frac{R_1}{a^2}$$

$$= X_{eq2} = \frac{X_{eq1}}{a^2} = X_{l2} + X_{l1}'$$

$$X_{l2} + \frac{X_{l1}}{a^2}$$

$$V_1' = \frac{V_1}{a}, I_1' = I_2 = aI_1$$

Practical Transformer: Rating

- Rating: the condition under which a transformer is designed to operate continuously
- Determining factors:
 1. the voltage across its magnetizing inductance (the maximum flux density before saturation of the magnetic material of the core)
 2. the maximum current that a winding can tolerate without overheating (temperature limit of insulation and the cooling methods)
- Apparent power: S_{rated}
- Nameplate: $S_{\text{rated}}, V_{1\text{rated}}/V_{2\text{rated}}, \text{frequency}$

Practical Transformer Ratings: Example

HV → 1
LV → 2

The low voltage winding of a 500 kVA, 69/4.16 kV, 60 Hz transformer has 25 turns of the wire. Calculate:
N₂

1. The rated current of the transformer
2. The number of turns of the high voltage winding N₁
3. The maximum flux within the core, if the transformer operates off its rated voltage

$$\textcircled{1} \quad I_{1,\text{rated}} = \frac{\text{Rated}}{V_{1,\text{rated}}} = \frac{500 \text{ kVA}}{69 \text{ kV}} = 7.25 \text{ A} \quad \begin{matrix} \text{rated current of} \\ \text{the HV side} \end{matrix}$$

$$I_{2,\text{rated}} = \frac{\text{Rated}}{V_{2,\text{rated}}} = \frac{500 \text{ kVA}}{4.16 \text{ kV}} = 120 \text{ A} \quad \begin{matrix} \text{rated current of} \\ \text{LV side} \end{matrix}$$

$$\textcircled{2} \quad \frac{N_1}{N_2} = \frac{V_1}{V_2} \Rightarrow N_1 = N_2 \left(\frac{V_1}{V_2} \right) = 25 \left(\frac{69}{4.16} \right) = 415 \text{ turns}$$

high voltage winding turns

Practical Transformer Ratings: Example

The low voltage winding of a 500 kVA, $69/4.16 \text{ kV}$, 60 Hz transformer has 25 turns of the wire. Calculate:

1. The rated current of the transformer
2. The number of turns of the high voltage winding
3. The maximum flux within the core, if the transformer operates off its rated voltage Φ_m

$$\phi = \Phi_m \sin \omega t$$

$$v_i = N_1 \frac{d\phi}{dt} = N_1 \frac{d}{dt} [\Phi_m \sin \omega t]$$

$$= N_1 \Phi_m \cos(\omega t) (\omega)$$


$$v_i = (N_1 \Phi_m \omega) \cos(\omega t)$$

peak of $v_i \Rightarrow V_{i, \text{peak}}$

$$V_{i, \text{peak}} = N_1 \Phi_m (2\pi f)$$

$$\Phi_m = \frac{V_{i, \text{peak}}}{N_1 (2\pi f)}$$
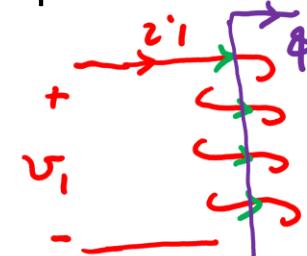
$$= \frac{\sqrt{2} \times 69 \times 10^3}{415 \times (2\pi \times 60)} = 0.624 \text{ Weber (wb)}$$



$$f = F_m \cos(\omega t \pm \varphi)$$

Practical Transformer Voltage Regulation

and Efficiency

$$\bar{I}_2 = I_2 \angle \theta_2$$

$$\bar{R}_{eq2} \rightarrow V_2$$

nature of load


lagging p.f. load

leading p.f. load

$$P.F. = \cos \theta_2$$


$$\bar{I}_2 = |S| \frac{V_2}{V_2} \angle -\theta_2$$

$$\bar{V}_2 = V_2 \angle 0^\circ$$

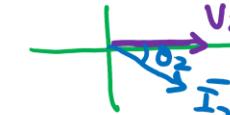

Voltage Regulation: most loads connected to the secondary of a transformer are designed to operate at essentially constant voltage. However, as the current is drawn through the transformer, the load terminal voltage changes because of the voltage drop in the internal impedance of the transformer. The load terminal voltage may go up or down depending on the nature of the load. The large voltage change is not desirable for many loads. For example, as more and more light bulbs are connected to the transformer secondary and the voltage decreases appreciably, the bulbs will glow with diminished illumination. To reduce the magnitude of the voltage change, the transformer should be designed for a low value of the internal impedance Z_{eq} .
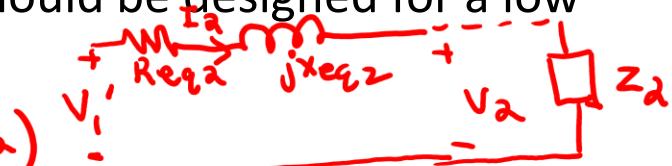
$$\bar{V}'_1 = \bar{V}_2 + \bar{I}_2 (R_{eq2} + jX_{eq2})$$



Voltage regulation is used to identify voltage change in the transformer with loading R_{eq1} jX_{eq1}



$$V_1 = V_2' + I_2' [R_{eq1} + jX_{eq1}]$$


Voltage Regulation =

$$\frac{|V_2|_{NL} - |V_2|_L}{|V_2|_L}$$

+ve
-ve

$V_1' > V_2$ (lagging p.f. load)
 $V_1' < V_2$ (leading p.f. load)

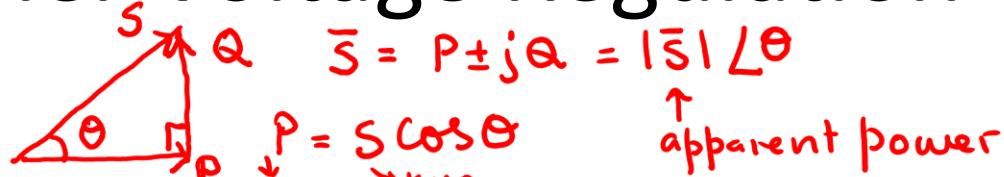Practical Transformer Voltage Regulation and Efficiency



Efficiency: losses in the transformer are small because the transformer is a static device and there are no rotational losses such as windage and friction losses in a rotating machine. In a well designed transformer the efficiency can be as high as 99%.

Efficiency = $\frac{\text{Output Power } (P_{out})}{\text{Input Power } (P_{in})} = \frac{P_{out}}{P_{out} + \text{losses}} = \frac{P_{in} - \text{losses}}{P_{in}}$

P_{out} = V₂I₂cosθ₂ → phase angle b/w V₂ and I₂

losses = core loss (P_c) + Copper losses (P_{cu})

P_{core loss} = $\frac{(V_1)^2}{R_C}$

P_{cu} = I₁²R₁ + I₂²R₂

P_{cu} = I₁²R_{eq1} = I₁²[R₁ + a²R₂]

P_{cu} = I₂²R_{eq2} = I₂²[R₂ + $\frac{R_1}{a^2}$]

Equivalent circuit, Voltage regulation and Efficiency


HV → 1
LV → 2

A 1-phase, 100 kVA, 11000/2200 V, 60 Hz transformer has the following parameters:

$R_{HV} = 6 \Omega$, $L_{HV} = 0.08 H$, $L_m(HV) = 160 H$, $R_{C(HV)} = 125 k\Omega$, $R_{LV} = 0.28 \Omega$, $L_{LV} = 0.0032 H$. Obtain an equivalent circuit of the transformer

1. Referred to the high voltage side
2. Referred to the low voltage side

slide #16

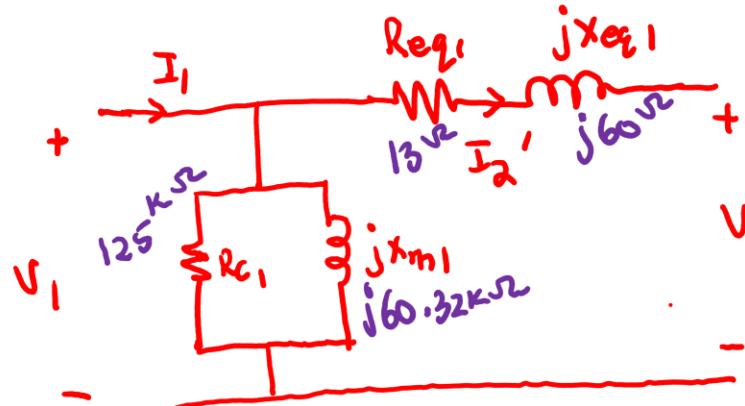

$$V_2' = \alpha V_1 = 5 \times 2200 = 11000 V$$

$$I_1 = \frac{100 \text{ kVA}}{11 \text{ kV}} = 9.09 \text{ A} = I_2'$$

$$R_{req1} = R_1 + \alpha^2 R_2$$

$$\alpha = \frac{N_1}{N_2} = \frac{V_1}{V_2'} = \frac{11000}{2200}$$

$$\alpha = 5$$

$$R_{req1} = 6 + [(5^2) \times 0.28] = 13 \Omega$$

$$X_{req1} = X_1 + \alpha^2 X_2$$

$$= 30.16 + [5^2 \times 1.21] = 60 \Omega$$

$$R_1 = 6 \Omega$$

$$R_2 = 0.28 \Omega$$

$$X_1 = 2\pi(60)(0.08) = 30.16 \Omega$$

$$L_1 = 0.08 H$$

$$X_2 = 1.21 \Omega$$

$$L_2 = 0.0032 H$$

$$L_{m1} = 160 H$$

$$R_{C1} = 125 k\Omega$$

$$X_{m1} = 2\pi(60)(160) = 60319 \Omega$$

$$= 60 k\Omega$$

Equivalent circuit, Voltage regulation and Efficiency

A 1-phase, 100 kVA, 11000/2200 V, 60 Hz transformer has the following parameters:

$$R_{HV} = 6 \Omega, L_{HV} = 0.08 \text{ H}, L_{m(HV)} = 160 \text{ H}, R_{C(HV)} = 125 \text{ k}\Omega, R_{LV} = 0.28 \Omega, LLV = 0.0032 \text{ H.}$$

Obtain an equivalent circuit of the transformer

1. Referred to the high voltage side
2. Referred to the low voltage side

Equivalent circuit, Voltage regulation and Efficiency

$\begin{matrix} 1 \\ \text{H.V} \end{matrix}$ $\begin{matrix} 2 \\ \text{L.V} \end{matrix}$

$$R_{eq2} = \frac{R_1}{A^2} + R_2 = 0.104 \Omega$$

$$X_{eq2} = 0.313 \Omega$$

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq} = 0.104 \Omega$, $X_{eq} = 0.313 \Omega$ referred to low voltage side. If the transformer supplies a 10 kVA, 220 V load whose power factor is 0.85 (lagging), determine

1. The Voltage Regulation

Slide # 20

$$\cos \theta = 0.85$$

$$\theta = 31.79^\circ$$

$$\% VR = \frac{|V'_1| - |V_2|}{|V_{al}|} \times 100\%.$$

$|V_2|$ = rated L.V side voltage = 220 V

$$\bar{V}'_1 = \bar{V}_2 + [\bar{I}_2 (0.104 + j0.313)]$$

$$= 220 \angle 0^\circ + [(45.4 \angle -31.79^\circ) (0.104 + j0.313)]$$

$$\bar{V}'_1 = 231.7 \angle 2.37^\circ V$$


$$\% VR = \frac{231.7 - 220}{220} \times 100\% = 5.3\%$$

$$V'_1 = \underline{\hspace{10cm}}$$

$$\bar{V}_2 = 220 \angle 0^\circ V$$

$$\bar{I}_2 = \frac{10 \text{ kVA}}{220 \text{ V}} \angle -31.79^\circ$$
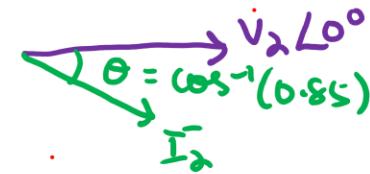
$$\bar{I}_2 = 45.4 \angle -31.79^\circ A$$



Equivalent circuit, Voltage regulation and Efficiency

$$R_{eq1} = 10.4 \Omega$$

$$X_{eq1} = 31.3 \Omega$$

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq} = 10.4 \Omega$, $X_{eq} = 31.3 \Omega$ referred to high voltage side. The core loss is 100 W at rated terminal voltage. The transformer is providing 75% of the full load with load power factor 0.6 (lagging), determine

$$\alpha = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{2200}{220} = 10$$


$$V_2' = \alpha V_2 = 2200 \quad I_a' = \frac{I_2}{\alpha}$$

1. The Efficiency
2. The value of the maximum efficiency
3. The transformer power output at the maximum efficiency

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$P_{in} = P_{out} + P_{core} + P_{cu}$$

$$P_{out} = V_2' I_2' \cos \theta_2$$

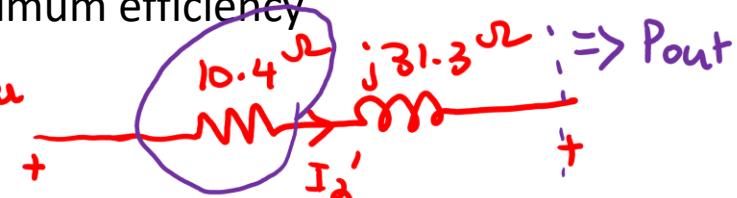

$$V_1 \quad P_{cu} = (I_2')^2 \times 10.4$$

$$- \quad P_{cu} = (3.41)^2 \times 10.4 = 1121 \text{ W}$$

$$\eta = \frac{(P_{out} + P_{core} + P_{cu})}{(P_{out} + P_{core} + P_{cu})} \times 100\%$$

$$\eta = \frac{(2200 \times 3.41 \times 0.6)}{(2200 \times 3.41 \times 0.6) + 100 + 1121} \times 100\% = 95.32\%$$

Equivalent circuit, Voltage regulation and Efficiency

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq} = 10.4 \Omega$, $X_{eq} = 31.3 \Omega$ referred to high voltage side. The core loss is 100 W at rated terminal voltage. The transformer is providing 75% of the full load with load power factor 0.6 (lagging), determine

The value of the maximum efficiency

$$\eta_{max} \text{ occurs @ } \begin{cases} P_{Cu} = P_{core} \\ \cos \theta_2 = 1 \end{cases}$$

$$\eta_{max} = \frac{V_2' I_2'' \cos \theta_2}{[V_2' I_2'' \cos \theta_2] + P_{core} + P_{Cu}} \times 100\%$$

$$= \frac{2200 \times 3.1 \times 1}{[2200 \times 3.1 \times 1] + 100 + 100} \times 100\% = 97\%$$

$$\begin{aligned} P_{Cu} &= 100 \text{ W} \\ (I_2'')^2 \times 10.4 &= 100 \\ I_2'' &= \sqrt{\frac{100}{10.4}} \\ &= 3.1 \text{ A} \end{aligned}$$

@ unity p.f.

to deliver max. η , the transformer should be loaded at $\frac{6820}{10000} = 68.2\%$.

Equivalent circuit, Voltage regulation and Efficiency

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq} = 10.4 \Omega$, $X_{eq} = 31.3 \Omega$ referred to high voltage side. The core loss is 100 W at rated terminal voltage. The transformer is providing 75% of the full load with load power factor 0.6 (lagging), determine

The transformer power output at the maximum efficiency

$$P_{our} | = 2200 \times 3.1 \times 1 = 6820 \text{ W}$$

$$\eta = \eta_{max}$$