

Electric Circuits Variables and Components

Electric Circuit or Network

- Network - Interconnection of two or more circuit elements
- Electric Circuit – if the network contains at least one closed path, it is also an electric circuit

Units - SI System (International System of Units)

Base units:

Base Quantity	Name	Symbol
length	meter	m
mass	kilogram	kg
time	second	s
electric current	ampere	A
thermodynamic temperature	kelvin	K
amount of substance	mole	mol
luminous intensity	candela	cd

Derived units:

- work or energy: joule (J) $\rightarrow 1 \text{ J} = 1 \text{ kg m}^2 \text{ s}^{-2}$
- power (rate of doing work): watt (W) $\rightarrow 1 \text{ W} = 1 \text{ J/s}$

SI: Units and Prefixes

Any measurement can be expressed in terms of a unit, or a unit with a “prefix” modifier.

FACTOR	NAME	SYMBOL
10^{-9}	nano	n
10^{-6}	micro	μ
10^{-3}	milli	m
10^3	kilo	k
10^6	mega	M

Example: $12.3 \text{ mW} = 0.0123 \text{ W} = 1.23 \times 10^{-2} \text{ W}$

Electric Circuit Variables

- Charge
- Current
- Voltage
- Power and Energy

Circuit Variable - Charge


- Law of conservation of charge - Charge cannot be created or destroyed, only transferred
- Matter is made of atoms, each atom consist of electrons (negative charge), protons (positive charge), and neutrons
- Charge symbol is Q or q
- In SI system, the fundamental unit of charge is **Coulomb (C)**. It is defined in terms of Amperes
- Counts the number of electrons (or positive charges) present
- Charge on a single electron is $-1.602 \times 10^{-19} \text{ C}$
- One Coulomb is large unit for charge, 6.24×10^{18} electrons
- Charge is always multiple of electron charge

Circuit Variables - Current and Charge

Coulomb is defined in terms of **Ampere** by counting the total charge that passes through an arbitrary cross section of a wire during an interval of one second

Charge in Motion - **Current** is the rate of charge flow:
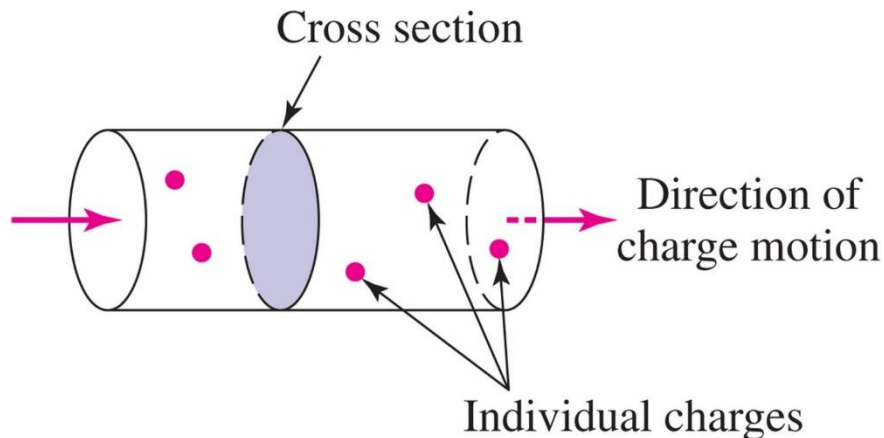
$$1 \text{ ampere} = 1 \text{ coulomb/second (or } 1 \text{ A} = 1 \text{ C/s)}$$



Circuit Variables - Current and Charge

Current (designated by I or i) is the rate of flow of charge in a specified direction



$$i = \frac{dq}{dt}$$

Current must be designated with both a direction and a magnitude


Unit – Ampere (A)

These two currents are the same:


$$Q = \int_{t_0}^t i \, dt$$

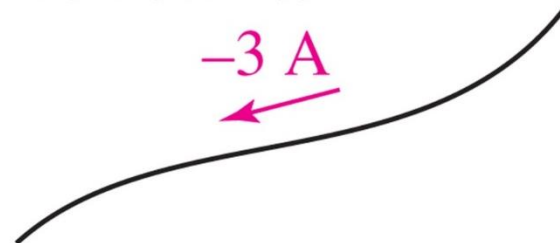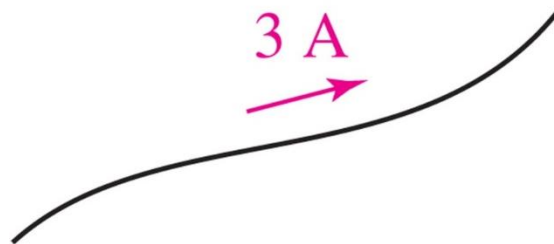


Circuit Variables - Current

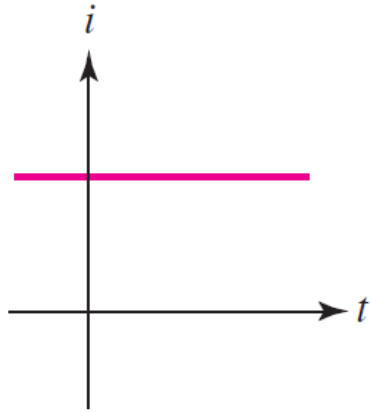


(a)

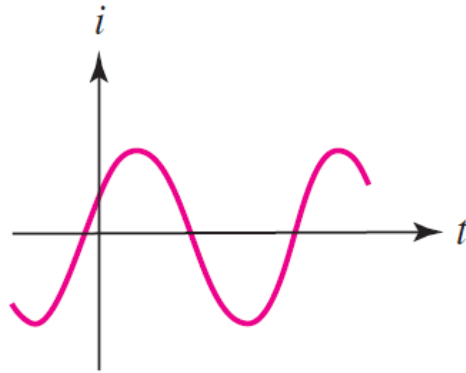

(b)

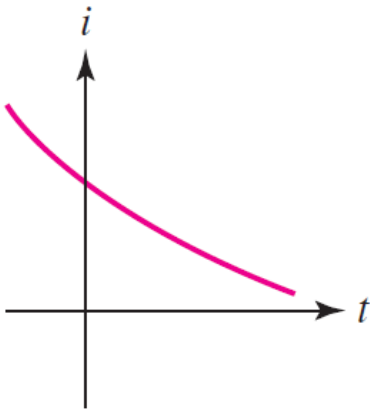

(c)

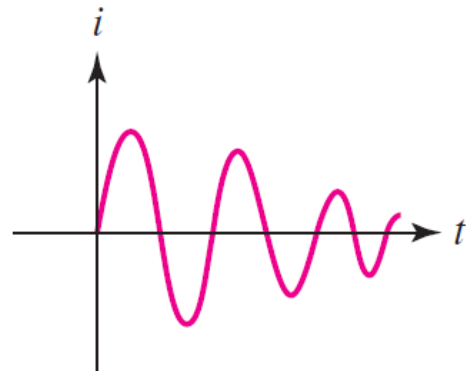


(d)

Circuit Variables - Current


PRACTICE

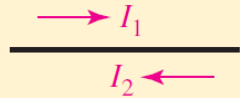2.4 In the wire of Fig. 2.7, electrons are moving *left to right* to create a current of 1 mA. Determine I_1 and I_2 .



■ **FIGURE 2.7**

Circuit Variable and Component - Voltage

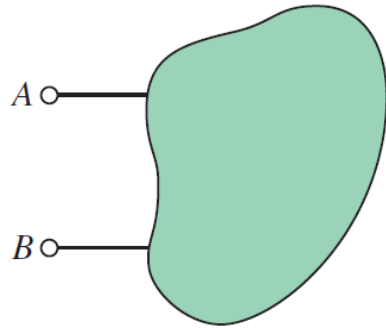

■ **FIGURE 2.8** A general two-terminal circuit element.

DC current enters terminal A, through the element and leaves out of terminal B

Pushing charge through this element requires energy – voltage or potential difference

Voltage across the two terminals is a measure of the work required to move charge through the element


Circuit Variable - Voltage

When 1 J of work is required to move 1 C of charge from A to B, there is a voltage of 1 volt between A and B.


Unit: volt and $1 \text{ V} = 1 \text{ J/C}$

Voltage (V or v) across an element requires both a magnitude and a polarity.


Example: (a)=(b), (c)=(d)

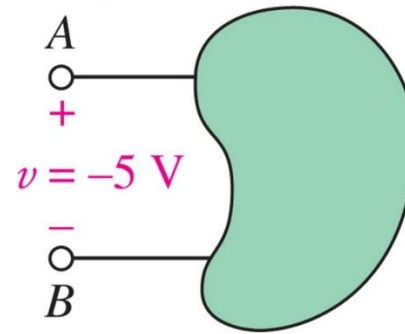


(a)

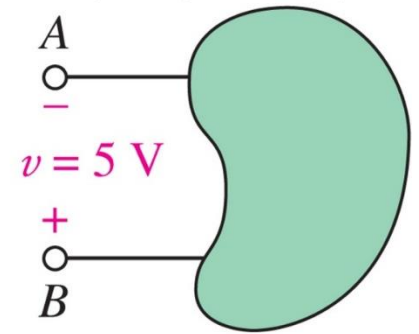

(b)

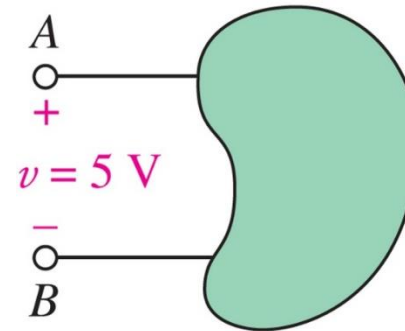

(c)

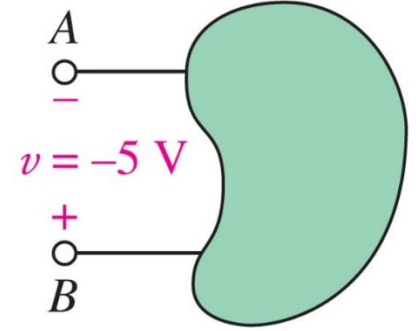


(d)

Circuit Variable - Voltage

PRACTICE

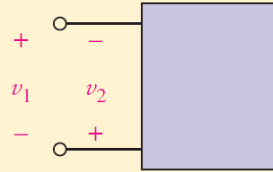2.5 For the element in Fig. 2.11, $v_1 = 17$ V. Determine v_2 .



■ FIGURE 2.11


Circuit Variable - Power: $p = vi$

The power required to push a current i (C/s) into a voltage v (J/C) is $p = vi$ (J/s = W). Unit – Watt (W)


Positive power – Power is absorbed by the element

Negative power – Power is supplied by the element

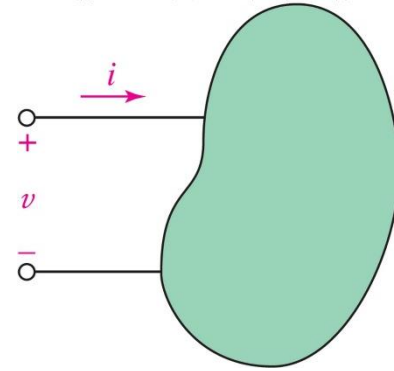Passive sign convention is satisfied if the direction of current is selected such that the current enters through positive terminal of the voltage and $p = +vi$ and if the current enters through the negative voltage terminal $p = -vi$




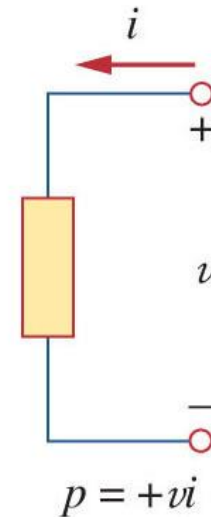Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

Absorbing Power

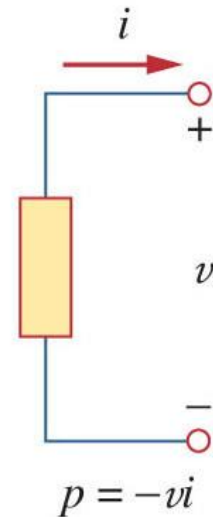


(b)

Supplying Power 14


Circuit Variable - Power

- Law of conservation of energy – algebraic sum of power in a circuit, at any instant of time, must be ZERO
- The sum of all power supplied must be absorbed by the other element


Example: Power Absorbed

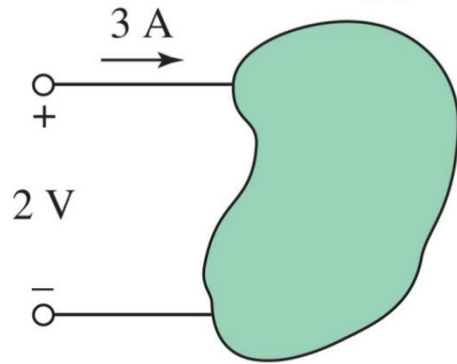

(a)

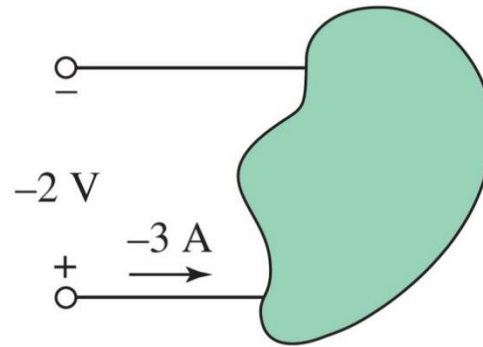

(b)

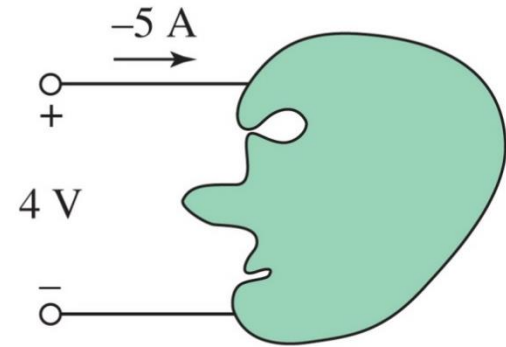

(c)

How much power is absorbed by the three elements above?

$$P_a = +6 \text{ W}, P_b = +6 \text{ W}, P_c = -20 \text{ W}.$$

(Note: (c) is actually supplying power)

Circuit Variable - Energy (W)

Power is rate of work or energy $p = \frac{dw}{dt}$

Energy is integral of power

$$w(t) = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$$

Energy determines total electricity need or how long your battery will last

Energy Example: Battery

Energy in units of joules (J) or watt-hours (Wh)

$$1 \text{ Wh} = 3600 \text{ J}$$

Battery capacity often given in amp-hours (Ah)

$$W = (\text{battery voltage}) \times (\text{capacity in Ah})$$


A 1.5 V battery with capacity of 2 Ah:

- Has total energy of 3 Wh = 10.8 kJ
- Can supply a circuit drawing 200 mA for 10 h

Circuit Components or Elements

A circuit element usually has two terminals (sometimes three or more).

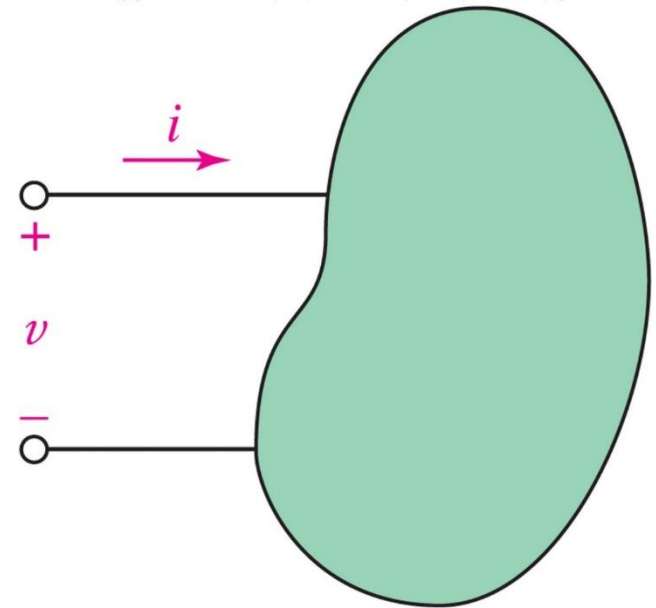The relationship between the voltage v across the terminals and the current i through the device defines the circuit element model.





Circuit Element - Voltage Sources

Independent Voltage Source:

An ideal voltage source is a circuit element that will maintain the specified voltage v_s across its terminals.

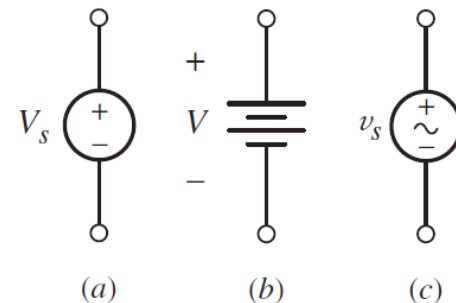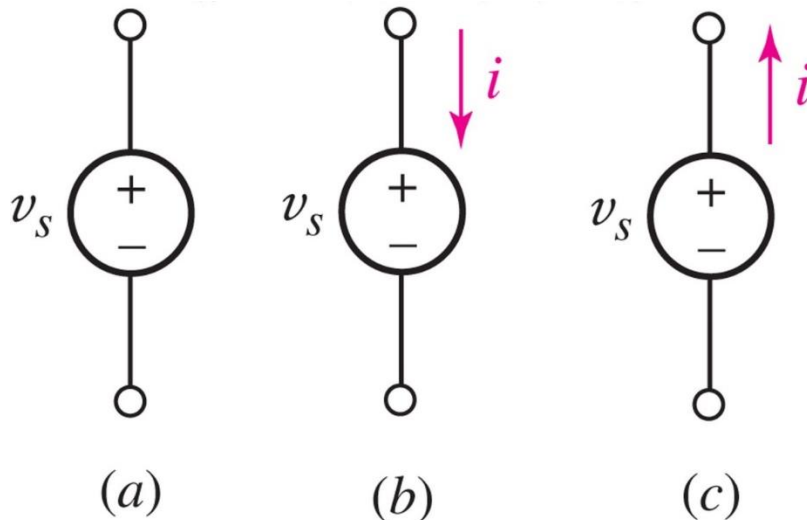The current will be determined by other circuit elements.




■ **FIGURE 2.16** (a) DC voltage source symbol; (b) battery symbol; (c) ac voltage source symbol.

Circuit Element - Current Sources

Independent Current Source

An ideal current source is a circuit element that maintains the specified current flow i_s through its terminals.

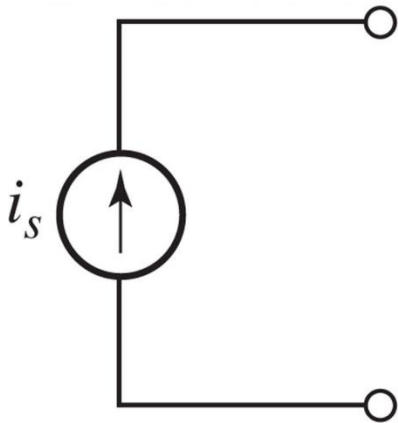
The voltage is determined by other circuit elements.




Dependent Sources

Dependent current sources (a) and (b) maintain a *current* specified by another circuit variable.

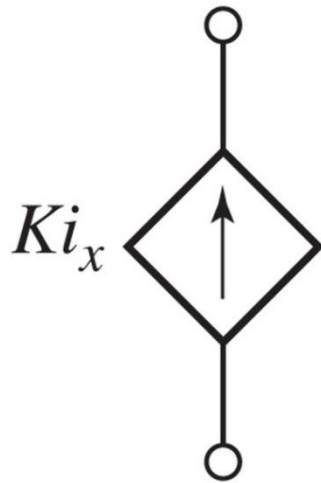
Dependent voltage sources (c) and (d) maintain a *voltage* specified by another circuit variable.




(a)

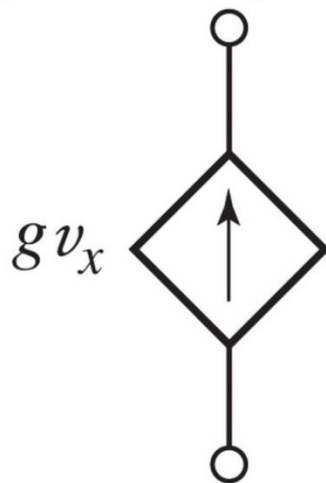

(b)

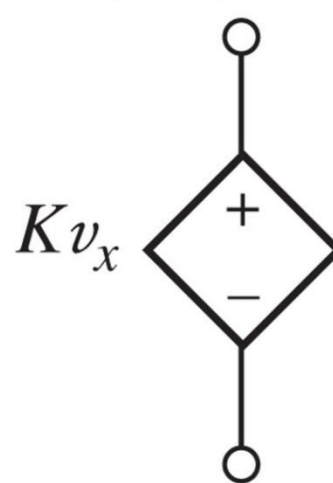

(c)

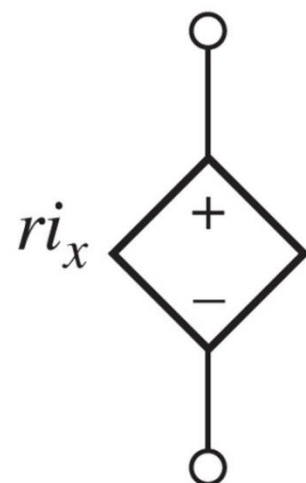


(d)

Example - Power

PRACTICE

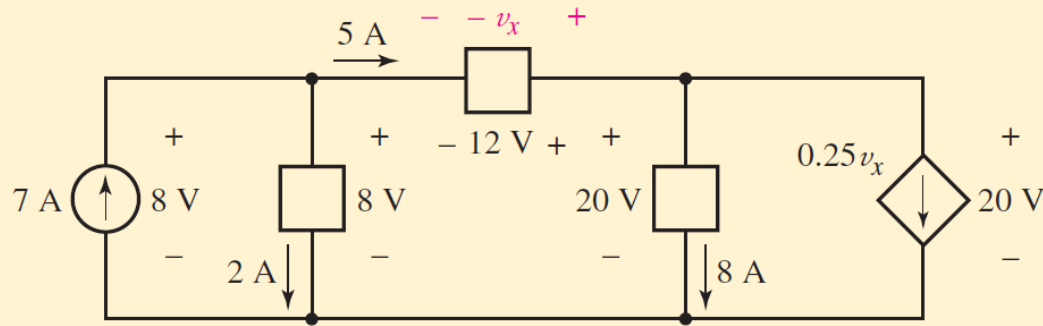2.9 Find the power *absorbed* by each element in the circuit in Fig. 2.20.



■ FIGURE 2.20

Resistance

Resistance (R) – is a property of a material to resist the flow of electric current

Resistance of an object is a function of its length, l , cross sectional area A and the material's resistivity


$$R = \rho \frac{l}{A}$$

The resistance is measured in Ohms (Ω)

Resistivity is in ohm-m


Good conductors, copper and aluminum, has low resistivities

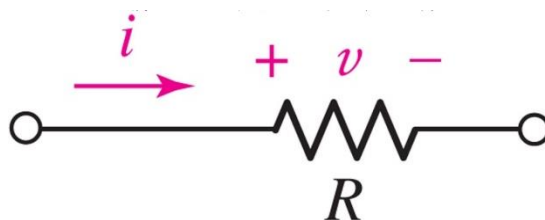Insulators, mica and paper, has high resistivities




Circuit Element - Resistor

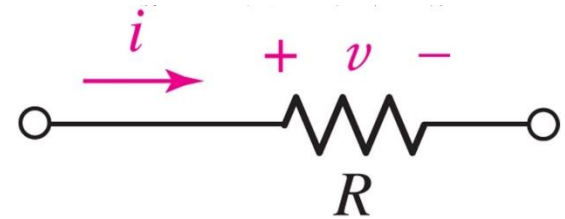Circuit element used to model the current resisting behaviour of a material is a RESISTOR.



Ohm's Law

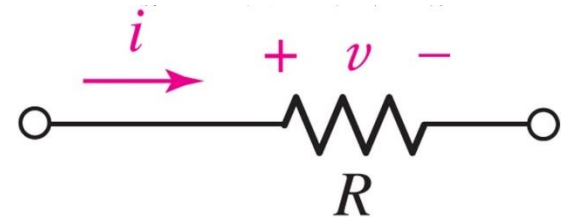

Power Absorption

Resistors absorb power: since $v = iR$

$$p = vi = v^2/R = i^2 R$$

Positive power means the device is absorbing energy.

Power is always positive for a resistor!



Example: Resistor Power

A $560\ \Omega$ resistor is connected to a circuit which causes a current of $42.4\ \text{mA}$ to flow through it.


Calculate the voltage across the resistor and the power it is dissipating.



Wire Gauge and Resistivity

The resistance of a wire is determined by the resistivity of the conductor as well as the geometry:

$$R = \rho l / A$$

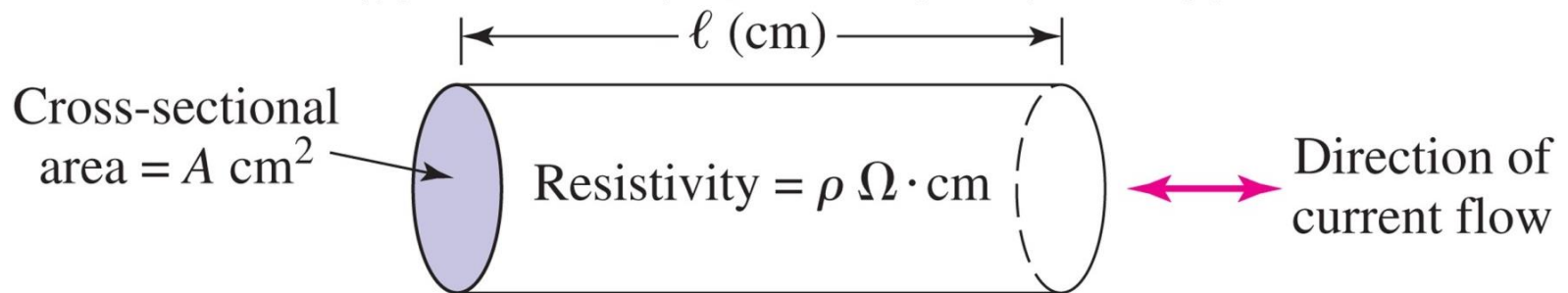

[In most cases, the resistance of wires can be assumed to be 0 ohms.]

Conductance

We sometimes prefer to work with *the reciprocal of resistance* ($1/R$), which is called conductance (symbol G , unit siemens (S)).

A resistor R has conductance $G = 1/R$.

Ohm's law (i - v equation) can be written as

$$i = Gv$$

Open and Short Circuits

An open circuit between A and B means $I = 0$.

Voltage across an open circuit: any value.

An open circuit is equivalent to $R = \infty \Omega$.

A short circuit between A and B means $v = 0$.

Current through a short circuit: any value.

A short circuit is equivalent to $R = 0 \Omega$.