


MT → Oct 16 → Wednesday → 4 pm to 6 pm

2 hrs → length

4 problems →  equivalent circuit of the transformer  
voltage regulation,  $\eta$  of the transformer  
DC generator  
DC motor

Formula sheet → will be posted on BB

# Electric Motors

Mid Term Review

A 1-phase, 100 kVA, 11000/2200 V, transformer has the following parameters:

$R_{HV} = 6 \Omega$ ,  $X_{HV} = 30.16 \Omega$ ,  $X_{m(HV)} = 60 \text{ k}\Omega$ ,  $R_{C(HV)} = 125 \text{ k}\Omega$ ,  $R_{LV} = 0.28 \Omega$ ,  $X_{LV} = 1.21 \Omega$ .

Obtain an equivalent circuit of the transformer

- ① Referred to the high voltage side
2. Referred to the low voltage side

$$R_1 = 6 \Omega$$

$$X_1 = 30.16 \Omega$$

$$R_2 = 0.28 \Omega$$

$$X_2 = 1.21 \Omega$$

$$X_{m1} = 60 \text{ k}\Omega$$

$$R_{C1} = 125 \text{ k}\Omega$$

$$R_{eq1} = R_1 + a^2 R_2$$


$$= 6 + (5^2 \times 0.28)$$

$$= 13 \Omega$$

$$X_{eq1} = X_1 + a^2 X_2 = 30.16 + (5^2 \times 1.21)$$

$$= 60.41 \Omega$$

$$11000 \text{ V} = V_1$$

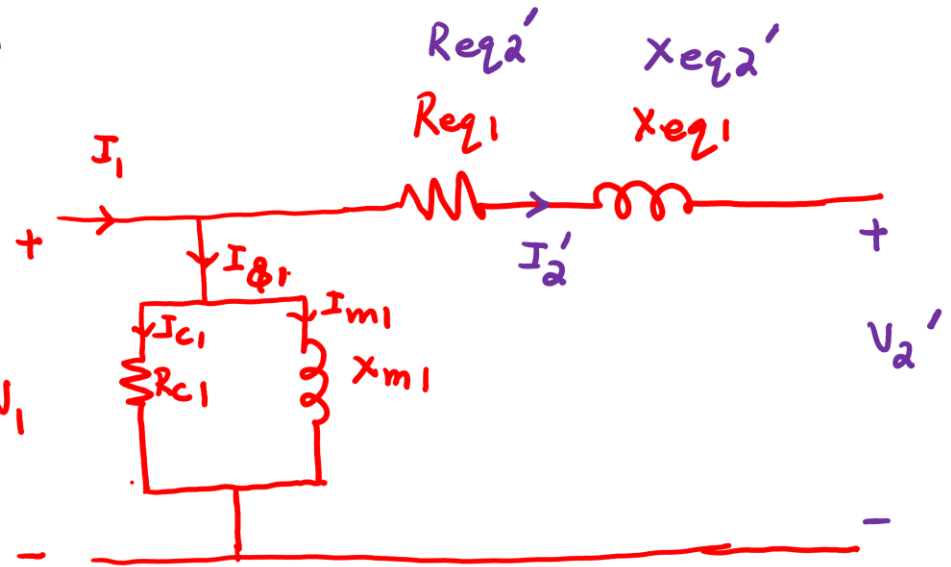

$$a = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{11000}{2200}$$

$$a = 5$$

$$\frac{V_1}{V_2} = a$$

$$V_2' = V_1 = a V_2 = 5 \times 2200 = 11000 \text{ V}$$

A 1-phase, 100 kVA, 11000/2200 V, transformer has the following parameters:

$R_{HV} = 6 \Omega$ ,  $X_{HV} = 30.16 \Omega$ ,  $X_{m(HV)} = 60 \text{ k}\Omega$ ,  $R_{C(HV)} = 125 \text{ k}\Omega$ ,  $R_{LV} = 0.28 \Omega$ ,  $X_{LV} = 1.21 \Omega$ .

Obtain an equivalent circuit of the transformer

1. Referred to the high voltage side

$$a = 5$$

2. Referred to the low voltage side


$$R_1 = 6 \Omega$$

$$X_1 = 30.16 \Omega$$

$$X_{m1} = 60 \text{ k}\Omega$$

$$R_{C1} = 125 \text{ k}\Omega$$
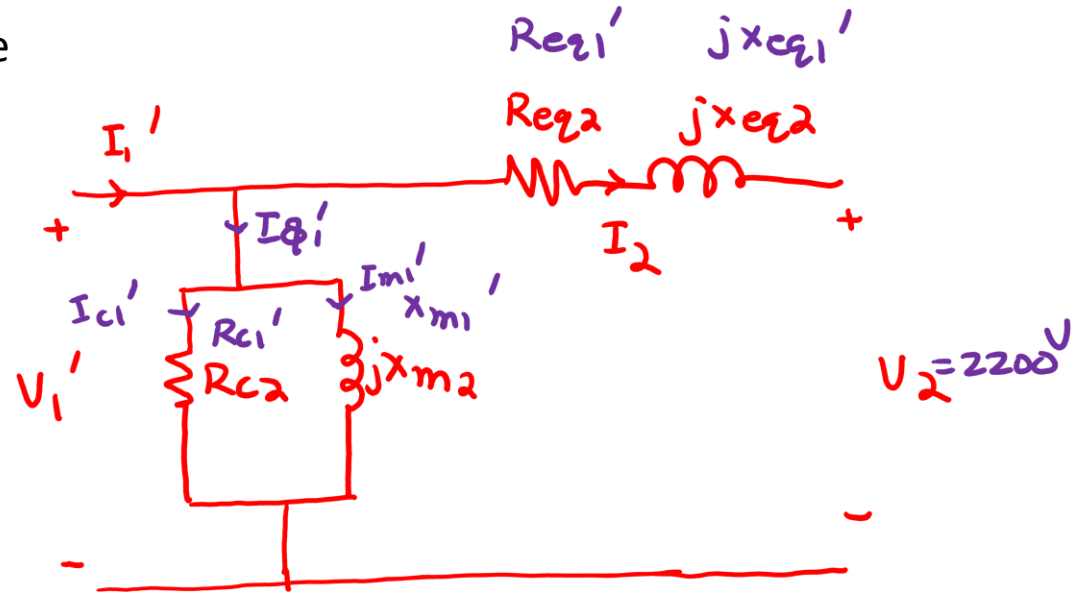
$$R_2 = 0.28 \Omega \quad X_2 = 1.21 \Omega$$



$$R_{eq2} = \frac{R_1}{a^2} + R_2 = \frac{6}{5^2} + 0.28 = 0.52 \Omega = \frac{R_{eq1}}{a^2}$$

$$X_{eq2} = \frac{X_1}{a^2} + X_2 = \frac{30.16}{5^2} + 1.21 = 2.42 \Omega$$

$$R_{C2} = R_{C1}' = \frac{R_{C1}}{a^2} = \frac{125 \text{ k}\Omega}{5^2} = 5 \text{ k}\Omega$$

$$X_{m2} = X_{m1}' = \frac{X_{m1}}{a^2} = \frac{60 \text{ k}\Omega}{5^2} = 2.4 \text{ k}\Omega$$


$$V_1' = V_a = \frac{V_1}{a} = 2200 \text{ V}$$

$$a = \frac{V_1}{V_2}$$

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq1} = 10.4 \Omega$ ,  $X_{eq1} = 31.3 \Omega$  referred to high voltage side. If the transformer supplies a 10 kVA, 220 V load whose power factor is 0.85 (lagging), determine

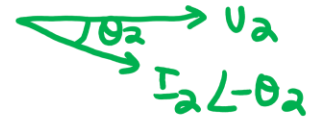1. The Voltage Regulation
2. The efficiency if the core loss 100 W is at the rated terminal voltage



$$R_{eq1} = 10.4 \Omega$$

$$X_{eq1} = 31.3 \Omega$$

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$VR = \frac{|V_1'| - |V_2|}{|V_2|} \times 100\%$$


$$|V_2| = 220V$$

$$\bar{V}_1' = \bar{V}_2 + \bar{I}_2 (R_{eq2} + jX_{eq2})$$

$$|I_2| = \frac{10000}{220} = 45.45 A$$

$$\bar{I}_2 = 45.45 \angle -31.78^\circ A$$

$$\cos^{-1}(0.85) = 31.78^\circ$$

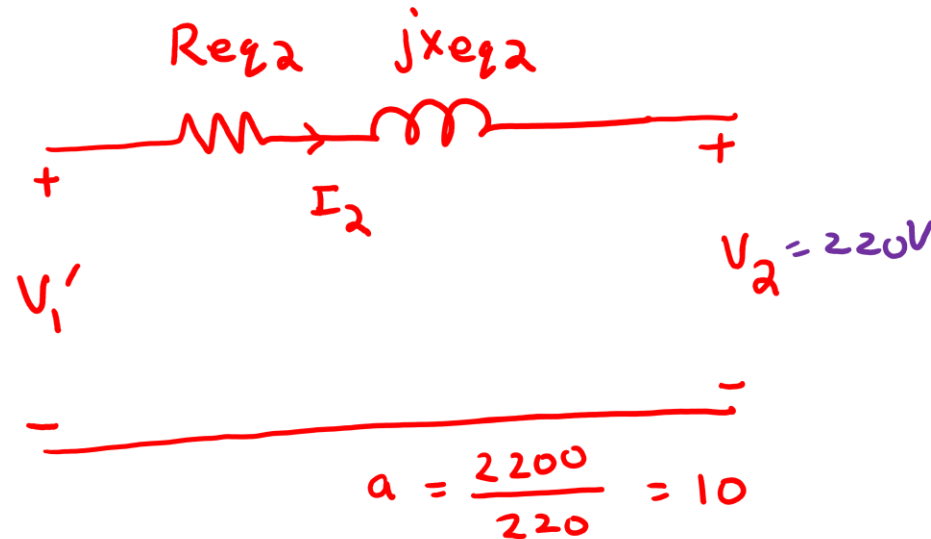

$$a = \frac{2200}{220} = 10$$

$$R_{eq2} = R_{eq1}' = \frac{R_{eq1}}{a^2} = \frac{10.4}{100} = 0.104 \Omega$$

$$X_{eq2} = \frac{31.3}{10^2} = 0.313 \Omega$$

A 1-phase, 10 kVA, 2200/220 V, 60 Hz transformer has the following parameters:

$R_{eq} = 10.4 \Omega$ ,  $X_{eq} = 31.3 \Omega$  referred to high voltage side. If the transformer supplies a 10 kVA, 220 V load whose power factor is 0.85 (lagging), determine

1. The Voltage Regulation
2. The efficiency if the core loss 100 W is at the rated terminal voltage

$$\bar{U}_1' = [220 \angle 0^\circ] + [(45.45 \angle -31.78^\circ)(0.104 + j0.313)]$$

$$\bar{U}_1' = 231.71 \angle 2.38^\circ \text{ V}$$

$$UR = \frac{231.71 - 220}{220} \times 100\% = 5.32\%$$

$$(2) \quad \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{out}}{P_{out} + P_{cu} + P_{core}} \times 100\%$$


$$P_{out} = \boxed{V_2 I_2 \cos \theta_2} = 10000 \times 0.85 = 8500 \text{ W}$$

$$P_{core} = 100 \text{ W}$$

$$P_{cu} = (I_2^2) R_{eq2} = (45.45)^2 \times 0.104 = 214.83 \text{ W}$$

$$\eta = \frac{8500}{8500 + 100 + 214.83} \times 100\% = 96.43\%$$
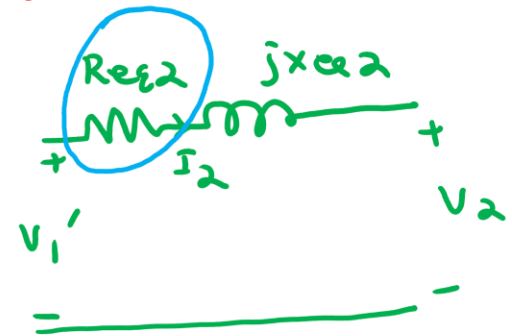
$$\begin{aligned} & \begin{array}{c} + \\ V_1' \\ - \end{array} \quad \begin{array}{c} \text{---} \\ R_c \\ \text{---} \end{array} \\ & P_{core} = \frac{V_1'^2}{R_c} \end{aligned}$$



In a DC machine the constant  $K_a$  is given by  $K_a = Z/2\pi$ , where  $Z$  is the total number of conductors in the armature. The armature winding has 40 coils each having 8 turns of wire. If the air gap flux per pole is 0.0293 Wb, what voltage will this machine generate if its shaft spun at 1000 rpm?

$N$

$$E_a = K_a \phi \omega$$

$$K_a = \frac{Z}{2\pi} = \frac{40 \times 8 \times 2}{2\pi} = 101.86$$

$$\omega = \frac{1000}{(60/2\pi)} \text{ rad/sec}$$



$$E_a = \left( \frac{320}{\pi} \right) (0.0293) \left( \frac{1000}{(60/2\pi)} \right)$$

$$E_a = 312.54 \text{ V}$$

The magnetization curve for a separately excited DC motor is given below (the magnetization curve is at 1500 rpm) and is running at 1200 rpm with  $I_a = 20$  A and  $I_f = 2.5$  A. The armature resistance  $R_a = 0.15 \Omega$ .

$I_f$ (A)	0	0.2	0.5	0.8	1.0	1.5	2.0	2.5	3.0	3.5	4.0	4.5	5.0	5.5
$E_a$ (V)	14	19	31	54	72	100	124	140	156	168	180	185	187	188

Calculate:

1. The voltage  $V_t$  applied to the armature circuit
2. The developed torque
3. The developed power

①  $V_t = E_a + I_a R_a$

$E_a \Big|_{1200} = ?$        $E_a \Big|_{1500 \text{ rpm}} = 140 \text{ V}$


$I_f = 2.5 \text{ A}$

$I_f = 2.5 \text{ A}$  [field current remains constant]

$E_a = k_a \Phi \omega \Rightarrow E_a \propto \omega \Rightarrow E_a \propto N$

$1500 \xrightarrow{\text{rpm}} 140 \text{ V}$   
 $1200 \text{ rpm} \rightarrow 140 \times \frac{1200}{1500} = 112 \text{ V}$

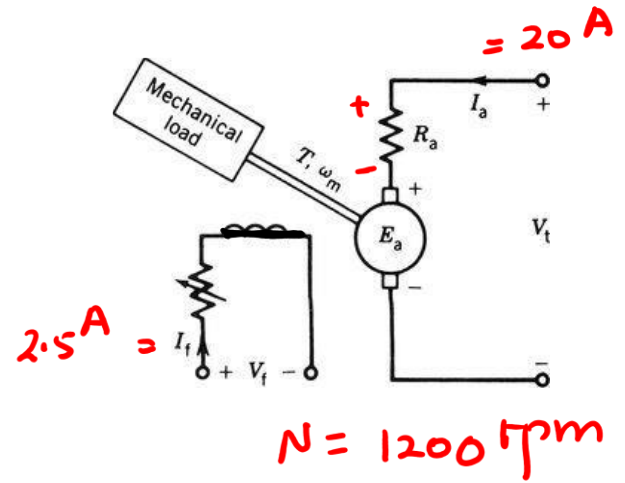$V_t = 112 + (20 \times 0.15)$   
 $V_t = 115 \text{ V}$



The magnetization curve for a separately excited DC motor is given below (the magnetization curve is at 1500 rpm) and is running at 1200 rpm with  $I_a = 20$  A and  $I_f = 2.5$  A. The armature resistance  $R_a = 0.15 \Omega$ .

$I_f$ (A)	0	0.2	0.5	0.8	1.0	1.5	2.0	2.5	3.0	3.5	4.0	4.5	5.0	5.5
$E$ (V)	14	19	31	54	72	100	124	140	156	168	180	185	187	188


Calculate:

1. The voltage  $V_t$  applied to the armature circuit
2. The developed torque
3. The developed power

$$\textcircled{2} \quad T = K_a \Phi i_a$$

$$E_a = K_a \Phi \omega \Rightarrow K_a \Phi = \frac{E_a}{\omega} = \frac{140}{(1500/9.55)} = \frac{112}{(1200/9.55)} = 0.8913$$
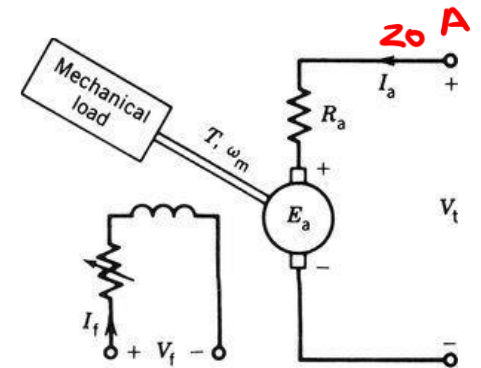
$$T = 0.8913 \times 20 = 17.83 \text{ N-m}$$






The magnetization curve for a separately excited DC motor is given below (the magnetization curve is at 1500 rpm) and is running at 1200 rpm with  $I_a = 20$  A and  $I_f = 2.5$  A. The armature resistance  $R_a = 0.15 \Omega$ .

$I_f$ (A)	0	0.2	0.5	0.8	1.0	1.5	2.0	2.5	3.0	3.5	4.0	4.5	5.0	5.5
$E$ (V)	14	19	31	54	72	100	124	140	156	168	180	185	187	188

Calculate:

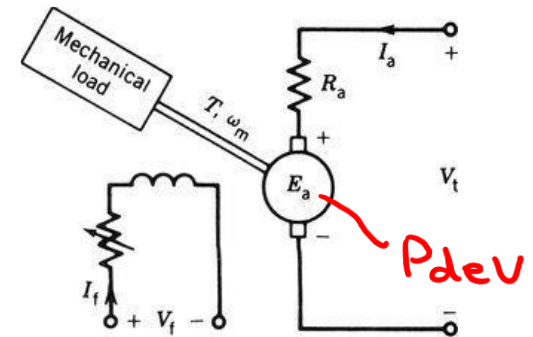1. The voltage  $V_t$  applied to the armature circuit
2. The developed torque
3. The developed power



$$P_{dev} = E_a I_a = 112 \times 20 = 2240 \text{ W}$$

$$= \omega T = \frac{1200}{(9.55)} \times 17.83 = 2240 \text{ W}$$