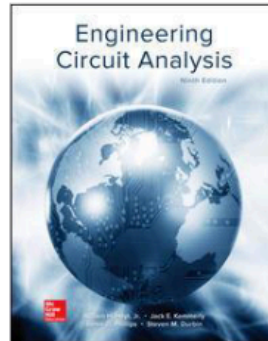


Lecture 8



November 24, 2023 12:15 AM

Sinusoids and Phasors



Sinusoids

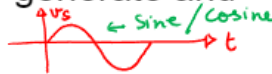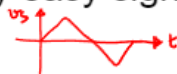- Sinusoids are interesting to us because there are a number of natural phenomenon that are sinusoidal in nature
- It is also a very easy signal to generate and transmit
- Also, through Fourier analysis, any practical periodic function can be made by adding sinusoids
- Lastly, they are very easy to handle mathematically



$$v(t) = V_m \sin \omega t$$

time-domain form

Sinusoids


Linear motion
velocity, v (m/sec)

- A sinusoidal forcing function produces both a transient and a steady state response
- When the transient has died out, we say the circuit is in sinusoidal steady state
- A sinusoidal voltage may be represented as:

value of v at any time t
↓ instantaneous value

$$v(t) = V_m \sin \omega t = V_m \sin \theta$$

$$= V_m \cos(\omega t - \pi/2)$$

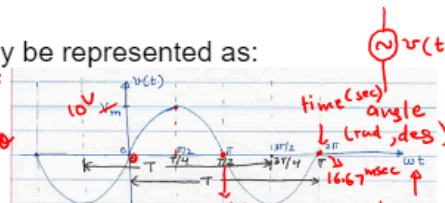

$v(t)$

Time (sec)
angle
 θ (rad, deg)

16.67 msec

v - instantaneous value

V_m - the amplitude of the sinusoid

ω - the angular frequency in rad/sec

| t | $v(t)$ | $\frac{\text{rad}}{(\omega)} \rightarrow \text{time (sec)}$ |
|-----|--------|---|
| 0 | 0 | |
| 4 | 10 | |
| 8 | 0 | |
| 12 | -10 | |
| 16 | 0 | |

Sinusoids


$$v(t) = V_m \sin \omega t$$

- The sinusoidal function repeats itself every T seconds
- This is called the period

$$T = \frac{2\pi}{\omega}$$

$$\omega T = 2\pi$$
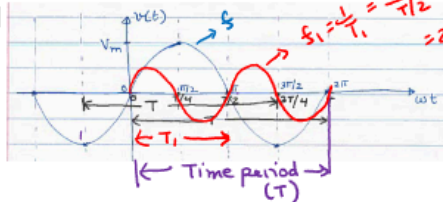
$$T = \frac{2\pi}{\omega} \rightarrow \text{rad} \rightarrow \text{rad/sec} \Rightarrow \text{sec}$$



- The period is inversely related to the frequency with units cycles per second, or Hertz (Hz)

$$f = \frac{1}{T} \rightarrow \text{Hz}$$

$$f = \frac{1}{(2\pi/\omega)} \Rightarrow \frac{\omega}{2\pi} \Rightarrow \omega = 2\pi f$$

$$\omega = 2\pi f \rightarrow \text{rad/sec}$$

Sinusoids

$v(t) \rightarrow$ time domain form of a sinusoid

Phase shift is used for expressing the relative timing of one wave versus another θ :



$$v(t) = V_m \sin(\omega t \pm \theta)$$

- Consider the three sinusoids:

$$v_1(t) = V_m \sin \omega t$$

$$v_2(t) = V_m \sin(\omega t + \theta)$$

$$v_3(t) = V_m \sin(\omega t - \theta)$$

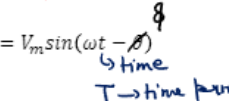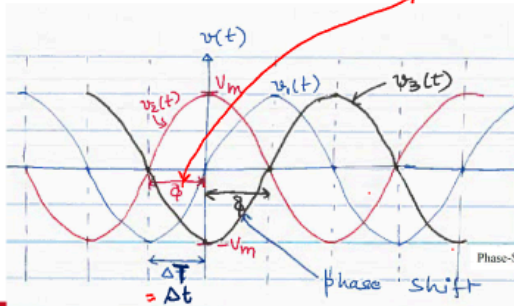

Phase Shift $\Rightarrow \theta = \frac{\pi}{4}, 2\pi$ (radians) $= \frac{\pi}{4}, 360^\circ$ (degrees)

Sinusoids – Problem Solving

For a sinusoid $v(t) = 5\sin(4\pi t - 60^\circ)$, calculate its amplitude, peak-to-peak value, phase, angular frequency, period and frequency.

$$v(t) = V_m \sin(\omega t - \theta)$$

$$V_m = 5V$$

$$\text{peak-to-peak value} = 10V$$

$$\text{phase} = 60^\circ$$



$$\omega = 4\pi \text{ rad/sec}$$


$$\omega T = 2\pi \Rightarrow T = \frac{2\pi}{4\pi} = \frac{1}{2} \text{ sec}$$

$$f = \frac{1}{T} = 2 \text{ Hz}$$



Steady State Response to Sinusoidal Sources

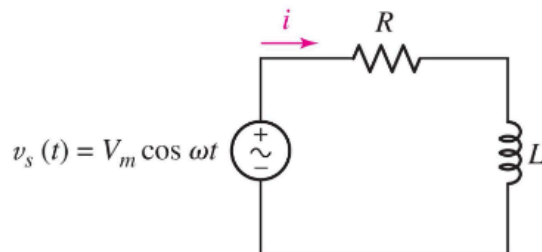When the source is sinusoidal, the transient/natural response is often ignored and only the "steady-state" response is considered.



Source is assumed to exist forever: $-\infty < t < \infty$

$\bar{V}, \vec{V}, \vec{V}$ Complex Numbers

$$v(t) = V_m \sin(\omega t \pm \theta)$$

- A powerful method for representing sinusoids is the **phasor**

- Phasor** is a complex number that represents the amplitude and phase of a Sinusoid $\bar{V} = V_m \angle \theta$ at $\omega = 2 \text{ rad/sec}$

- But in order to understand how they work, we need to cover some complex numbers first.

- A complex number z can be represented in rectangular form as:

$$z = x + jy \quad y = r \sin \theta$$

$$x = r \cos \theta$$

- It can also be written in polar or exponential form as:


$$z = r \angle \phi = r e^{j\phi}$$

$$r = \sqrt{x^2 + y^2}$$

$$\cos \theta = \frac{x}{r} \quad \sin \theta = \frac{y}{r}$$

$$\tan \theta = \frac{y}{x}$$

$$\theta = \tan^{-1}(y/x)$$

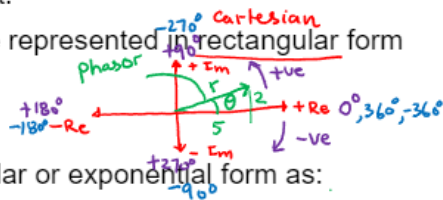

Complex Numbers

- The different forms can be interconverted
- Starting with rectangular form one can go to polar

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Imaginary axis




form, one can go to polar.

$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \frac{y}{x}$$

- Likewise, from polar to rectangular form goes as follows:
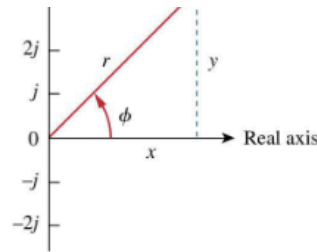
$$x = r \cos \phi \quad y = r \sin \phi$$



10

Complex Numbers

- The following mathematical operations are important.

• Addition

$$(x_1 + jy_1) + (x_2 + jy_2)$$

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$x_1 + x_2 + jy_1 + jy_2$$

• Multiplication

$$(r_1 \angle \theta_1)(r_2 \angle \theta_2)$$

$$z_1 z_2 = r_1 r_2 \angle (\theta_1 + \theta_2)$$

- Square Root

$$\sqrt{z} = \sqrt{r} \angle (\phi / 2)$$

• Subtraction

$$(x_1 + jy_1) - (x_2 + jy_2)$$

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$x_1 - x_2 + jy_1 - jy_2$$

• Division

$$\frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

- Complex Conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$


$$\bar{z} = x + jy = r \angle \phi$$

$$\bar{z}^* = x - jy = r \angle -\phi$$

- Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle (-\phi)$$
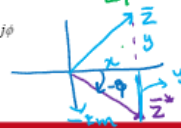
$$= \frac{1}{r \angle \phi} = \frac{1}{r} \angle -\phi$$



11

Phasors

- A sinusoid can be represented as the real component of a vector in the complex plane
- The length of the vector is the amplitude of the sinusoid
- The vector, V, in polar form, is at an angle ϕ with respect to the positive real axis

12

Sinusoid-Phasor Transformation


$$i(t) = I_m \cos(\omega t + \phi) \rightarrow \text{time-domain form}$$

$$\bar{I} = I_m e^{j\phi} = I_m \angle \phi \quad \left\{ \begin{array}{l} \text{phasor-domain} \\ \text{frequency-domain} \end{array} \right.$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$i(t) = \text{Re}\{I_m e^{j\omega t + \phi}\}$$

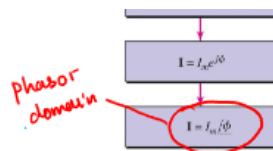The phasor representation of a current (or voltage) is in the frequency domain



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

TABLE 9.1

Sinusoid-phasor transformation.

Time domain representation

Phasor domain representation

$$V_m \cos(\omega t + \phi)$$

$$V_m / \phi$$

$$V_m \sin(\omega t + \phi) = V_m \cos(\omega t + \phi - 90^\circ)$$

$$V_m / \phi - 90^\circ$$

$$I_m \cos(\omega t + \theta)$$

$$I_m / \theta$$

$$I_m \sin(\omega t + \theta)$$

$$I_m / \theta - 90^\circ$$

$$\cos(\omega t + \phi - 90^\circ) = \sin(\omega t + \phi)$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\cos(A \pm 90^\circ) = \cos A \cos 90^\circ \mp \sin A \sin 90^\circ$$

$$\cos(A \pm 90^\circ) = 0 \mp \sin A = \mp \sin A$$

$$0 - \sin A = -\sin A$$

$$0 - \sin A = -\sin A$$

Sinusoid-Phasor Transformation

13

10.7 Transform each of the following functions of time into phasor form:

(a) $-5 \sin(580t - 110^\circ)$; (b) $3 \cos(600t) - 5 \sin(600t + 110^\circ)$; $\Rightarrow 5 \cos(600t + 110^\circ - 90^\circ)$

(c) $8 \cos(4t - 30^\circ) + 4 \sin(4t - 100^\circ)$. Hint: First convert each into a single cosine function with a positive magnitude.

Ans: $5 \angle -20^\circ$; $2.41 \angle -134.8^\circ$; $4.46 \angle -47.9^\circ$.

$$A + (-B) \checkmark$$

$$A - (+B)$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$\textcircled{a} -5 \sin(580t - 110^\circ) = 5 [-\sin(580t - 110^\circ)]$$

$$= 5 \cos(580t - 110^\circ + 90^\circ) = 5 \cos(580t - 20^\circ) = 5 \angle -20^\circ$$

$$\textcircled{b} 3 \angle 0^\circ - 5 \angle 20^\circ = 2.41 \angle -134.8^\circ = (1.694 - j1.71)$$



$$\textcircled{c} 8 \angle -30^\circ + 4 \angle -100^\circ - 90^\circ = 8 \angle -30^\circ + 4 \angle -190^\circ = 4.46 \angle -47.9^\circ$$

Phasors: The Resistor

15

In the frequency domain, Ohm's Law takes the same form:

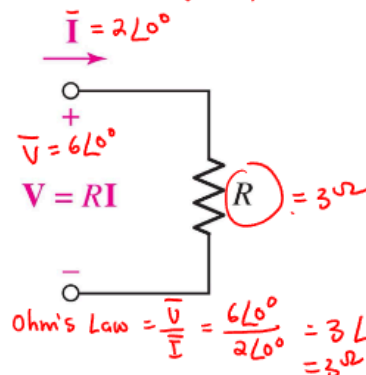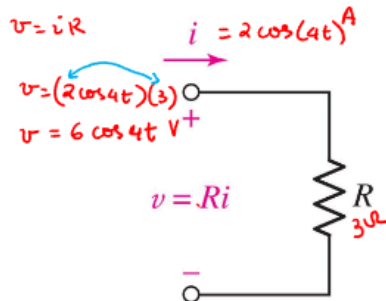
Voltage and current are in phase of a pure resistor



Phasors: The Inductor

16

$$v = L \frac{di}{dt}$$

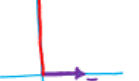


 $v = L \frac{di}{dt}$

$$v = 2 \frac{d}{dt} (2 \cos 4t) \\ = 16 [-\sin 4t]$$

$\vec{I} = 2 \angle 0^\circ \text{ A}$
 $\vec{V} = 16 \angle 90^\circ \text{ V}$
 $V = j\omega LI$
 $j(\omega)(L)$
 reactance, Ω
 Ohm's law $\frac{\vec{V}}{\vec{I}} = \frac{16 \angle 90^\circ}{2 \angle 0^\circ} = 8 \angle 90^\circ = 8j$

17

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$
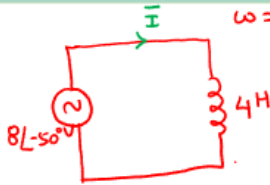
$$\omega = 100 \text{ rad/sec}$$


$$\bar{I} = 20 \angle -140^\circ \text{ mA}$$

$$i(t) = 0.02 \cos(100t - 140^\circ) \text{ A}$$

$$i(t) = 20 \cos(100t - 140^\circ) \text{ mA}$$

$$\frac{\bar{V}}{\bar{I}} = j\omega L$$

$$\frac{8 \angle -50^\circ}{\underline{I}} = j(100)(4)$$

$$\bar{I} = \frac{8 \angle -50^\circ}{400 \angle 90^\circ} = 0.02 \angle -140^\circ \text{ A}$$


18

$$i = C \frac{dv}{dt}$$

$$i = \frac{1}{2} \frac{d}{dt} [10 \cos 4t] = \frac{1}{2} \times 10 \times 4 [-\sin 4t] = 20 (-\sin 4t)$$

$$\mathbf{I} = j\omega C \mathbf{\bar{V}} \quad \text{20 } \omega = 14$$
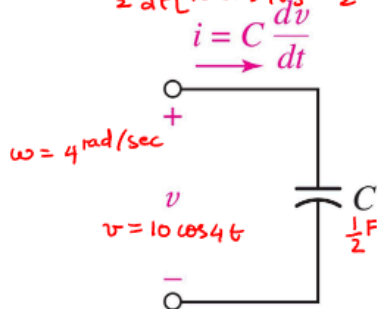
$$\longrightarrow \mathbf{\bar{I}} = 20 \angle 90^\circ$$




$$\frac{\bar{V}}{\bar{I}} = \frac{10 \angle 0^\circ}{20 \angle 90^\circ} = \frac{1}{2} \angle -90^\circ = -j \frac{1}{2} \Omega$$

Summary: Phasor Voltage/Current¹⁹

Relationships

$v(t) = V_m \cos(\omega t + \phi)$
 $v(t) = V_m \sin(\omega t + \phi)$


Time Domain

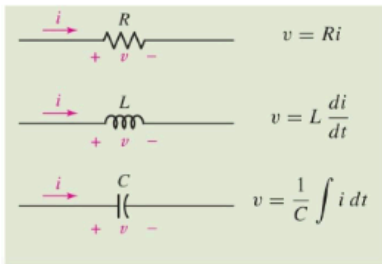

Calculus (hard but real)

$\hat{V} = V_m \angle \phi$
 $\hat{V} = V_m \angle \phi - 90^\circ$

Frequency Domain

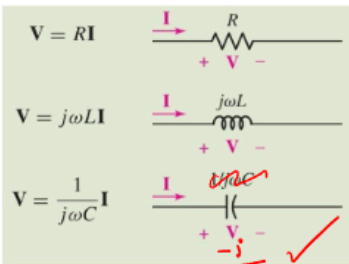

Algebra (easy but complex)

$j \times j = -1$
 $\frac{-j \times j}{(\omega C) \times j} = \frac{-(-1)}{j \omega C} = \frac{1}{j \omega C}$