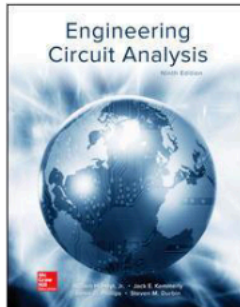


Lecture 9

November 24, 2023 12:18 AM

W9

AC Steady State Analysis



Sinusoid-Phasor Transformation

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

TABLE 9.1


Sinusoid-phasor transformation.

Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	V_m / ϕ
$V_m \sin(\omega t + \phi) = V_m \cos(\omega t + \phi - 90^\circ)$	$V_m / \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	I_m / θ
$I_m \sin(\omega t + \theta)$	$I_m / \theta - 90^\circ$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$


Summary: Phasor Voltage/Current Relationships

Time Domain

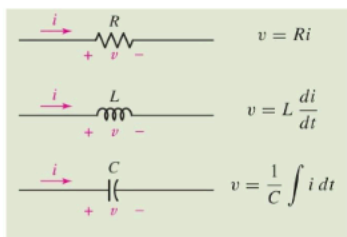

Calculus (hard but real)

Frequency Domain

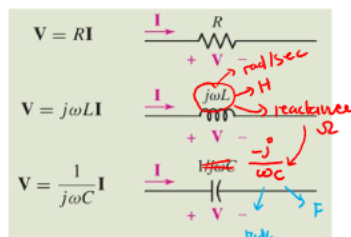

Algebra (easy but complex)


Kirchhoff's Laws for Phasors

Applying KVL in time implies KVL for phasors:

$$\bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_N = 0 \quad \text{complex \#s} \quad \bar{V}_i = |\bar{V}_i| \angle \pm \theta$$

Applying KCL in time implies KCL for phasors:
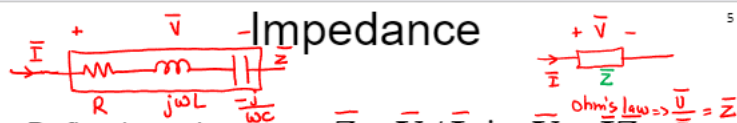
$$\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_N = 0$$



Define impedance as $\bar{Z} = \bar{V} / \bar{I}$, i.e. $\bar{V} = \bar{I}\bar{Z}$

$$\bar{Z} = R + j\omega L - j\left(\frac{1}{\omega C}\right) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$Z_R = R \quad Z_L = j\omega L \quad Z_C = 1/j\omega C$$

$$\bar{Z} = R + jX \quad (X_L > X_C) \Rightarrow \bar{Z} = R \pm jX$$

$$\bar{Z} = R - jX \quad (X_L < X_C)$$

Impedance is the equivalent of resistance in the frequency domain.


Impedance is a complex number (unit ohm). $\bar{Z}_T = \frac{1}{\frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2}}$

Impedances in series or parallel can be combined using "resistor rules."

$$R_T = R_1 + R_2 \quad \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$$

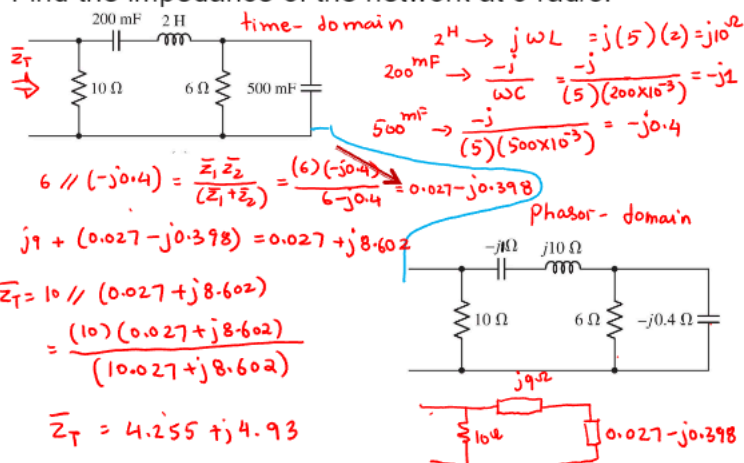
Example: Equivalent Impedance

Find the impedance of the network at 5 rad/s.



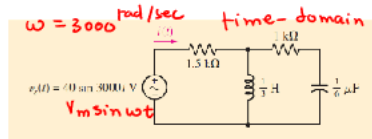Example: Equivalent Impedance and Ohm's Law

Find the current $i(t)$ in the following circuit.



$$v_s(t) = 40 \cos(3000t - 90^\circ)$$

$$\bar{V}_s = 40 \angle -90^\circ \text{ V}$$

$$\bar{Z}_T = 1.5 + [(j1) \parallel (1-j2)]$$


$$= 1.5 + \left[\frac{(j1)(1-j2)}{(1-j1)} \right]$$

$$\bar{Z}_T = (2 + j1.5) \Omega$$

$$\frac{1}{3} \text{ H} \rightarrow j(3000)\left(\frac{1}{3}\right) = j1000 \Omega = j1 \text{ k}\Omega$$

$$\frac{1}{6} \mu\text{F} \rightarrow \frac{-j}{(3000 \times \frac{1}{6} \times 10^{-6})}$$

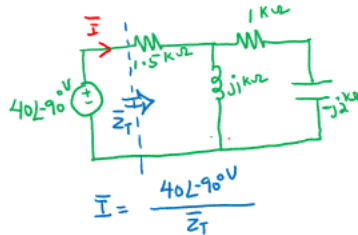
$$= -j2000 \Omega = -j2 \text{ k}\Omega$$



$$\bar{I} = \frac{40 \angle -90^\circ \text{ V}}{\bar{Z}_T}$$

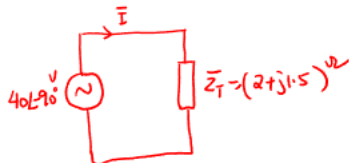Example: Equivalent Impedance and Ohm's Law

Find the current $i(t)$ in the following circuit.




$$\bar{I} = \frac{40 \angle -90^\circ \text{ V}}{(2 + j1.5) \text{ k}\Omega} = 16 \angle -126.87^\circ \text{ mA}$$

$$i(t) = 16 \cos(3000t - 126.87^\circ) \text{ mA}$$

$$i(t) = 16 \cos(3000t - 126.9^\circ) \text{ mA}$$

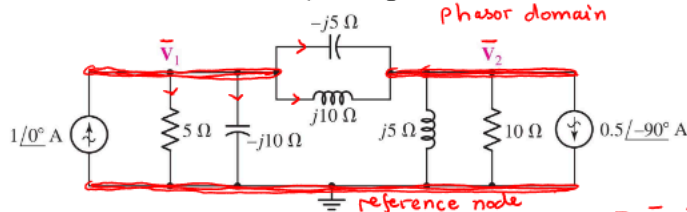Example: Nodal Analysis

Find the phasor voltages \bar{V}_1 and \bar{V}_2 .



$$(j10) \left[\frac{1 \angle 0^\circ}{5} - \left(\frac{\bar{V}_1 - 0}{-j5} \right) - \left[\frac{\bar{V}_1 - 0}{j10} \right] - \left[\frac{\bar{V}_1 - \bar{V}_2}{j10} \right] - \left[\frac{\bar{V}_1 - \bar{V}_2}{(-j5)} \right] \right] = 0$$


$$j10 - j2\bar{V}_1 - [-\bar{V}_1] - (\bar{V}_1 - \bar{V}_2) - (-2(\bar{V}_1 - \bar{V}_2)) = 0$$

$$j10 - j2\bar{V}_1 + \bar{V}_1 - \bar{V}_1 + \bar{V}_2 + 2(\bar{V}_1 - \bar{V}_2) = 0$$

$$-(2-j2)\bar{V}_1 + \bar{V}_2 = +j10 \quad \text{--- (1)}$$

Example: Nodal Analysis




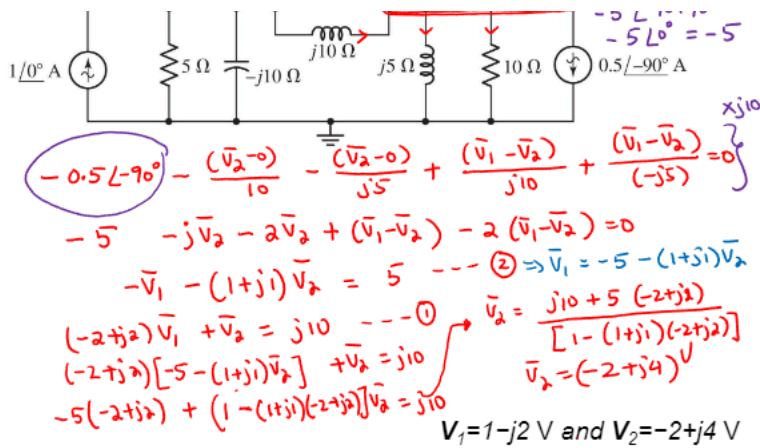

Superposition Example

12

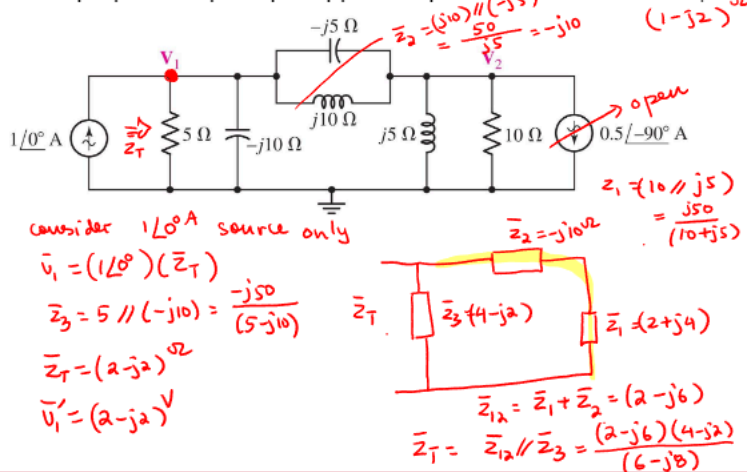
The superposition principle applies to phasors; use it to find V_1 .



Superposition Example

13

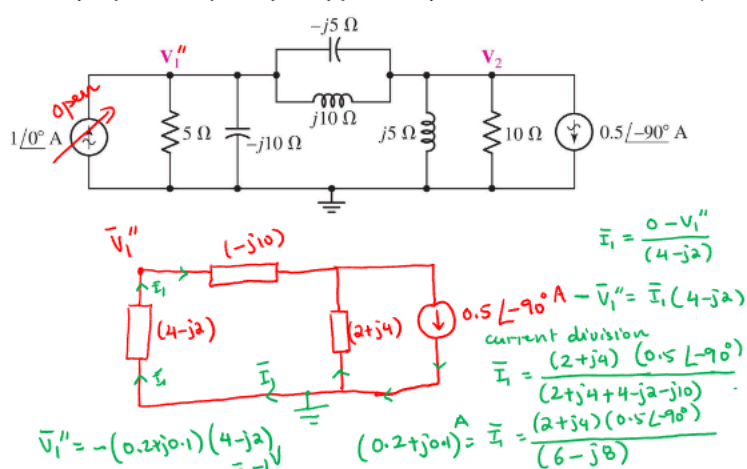
The superposition principle applies to phasors; use it to find V_1 .




Superposition Example

14

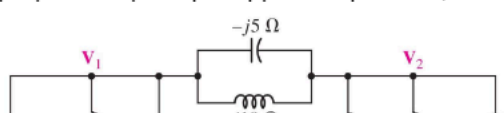The superposition principle applies to phasors; use it to find V_1 .



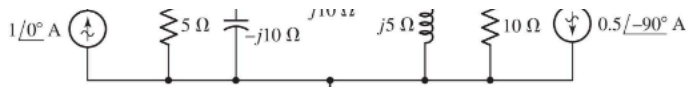

$$\bar{V}_1' = (2 - j2) V$$

$$\bar{V}_1'' = -1 V$$

$$\bar{V}_1 = \bar{V}_1' + \bar{V}_1'' = (2 - j2) - 1 = (1 - j2) V$$



$$V_1 = 1 - j2 V$$

Thévenin Example


15

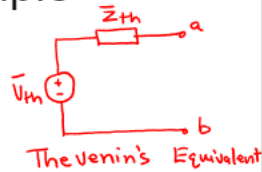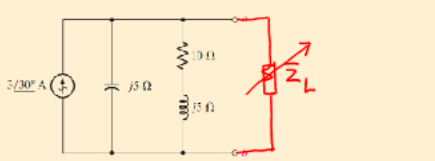10.15 For the circuit of Fig. 10.32, find the (a) open-circuit voltage \bar{V}_{ab} ; (b) downward current in a short circuit between a and b ; (c) Thévenin equivalent impedances \bar{Z}_{ab} in parallel with the current source.

Ans: $16.77 \angle -33.4^\circ V$, $2.60 \angle 1500 A$, $2.5 - j5 \Omega$.



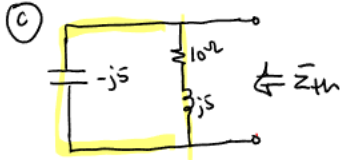\bar{Z}_{th} : turn off all independent sources, $3 \angle 30^\circ A \rightarrow$ open




$$\begin{aligned} \bar{Z}_{th} &= (10 + j5) \parallel (-j5) \\ &= \frac{(10 + j5)(-j5)}{10} \\ &= \frac{-j50 + 25}{10} = (2.5 - j5) \Omega \end{aligned}$$

Thévenin Example

16

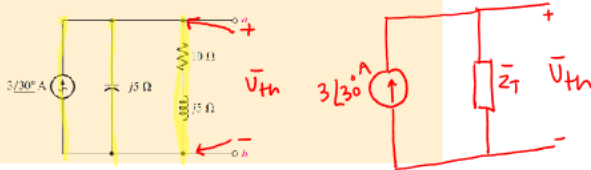10.15 For the circuit of Fig. 10.32, find the (a) open-circuit voltage \bar{V}_{ab} ; (b) downward current in a short circuit between a and b ; (c) Thévenin equivalent impedances \bar{Z}_{ab} in parallel with the current source.

Ans: $16.77 \angle -33.4^\circ V$, $2.60 \angle 1500 A$, $2.5 - j5 \Omega$.



(b)

Ohm's law

$$\bar{Z}_T = (-j5) \parallel (10 + j5) = 2.5 - j5$$


$$\begin{aligned} \bar{V}_{th} &= (3 \angle 30^\circ)(\bar{Z}_T) = (3 \angle 30^\circ)(2.5 - j5) \\ &= 16.77 \angle -33.43^\circ V \end{aligned}$$

Thévenin Example

17

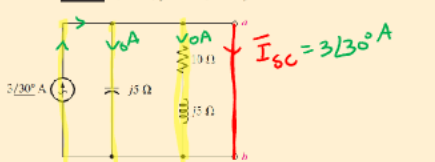
10.15 For the circuit of Fig. 10.32, find the (a) open-circuit voltage \bar{V}_{ab} ; (b) downward current in a short circuit between a and b ; (c) Thévenin equivalent impedances \bar{Z}_{ab} in parallel with the current source.

Ans: $16.77 \angle -33.4^\circ V$, $2.60 \angle 1500 A$, $2.5 - j5 \Omega$.



Phasor Diagrams


18

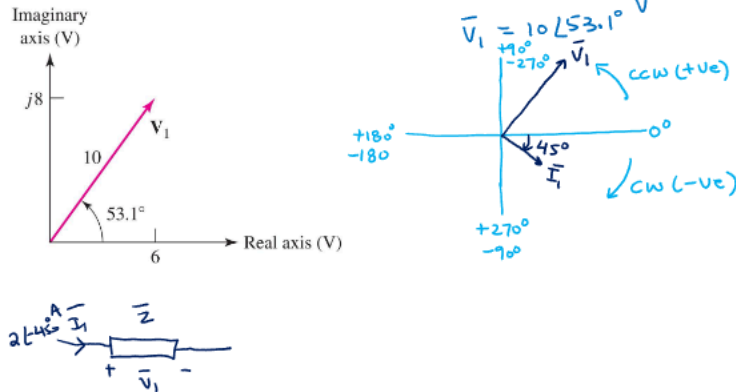

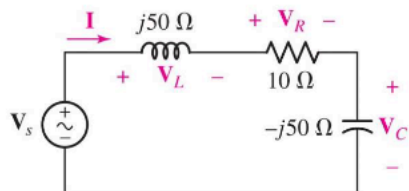Example Phasor Diagram

19

If we assume $\bar{I} = 1 \angle 0^\circ \text{ A}$



$$\bar{V}_s = \bar{I} \bar{Z}_T = (1 \angle 0^\circ)(10 + j50 - j50)$$

$$\bar{V}_s = 10 \angle 0^\circ \text{ V}$$


\bar{V}_s and \bar{I} are in phase

$$\bar{V}_R = R \bar{I} = 10 \angle 0^\circ \text{ V}$$

$$\bar{V}_C = \bar{I}(-j50)$$

$$= (1 \angle 0^\circ)(50 \angle -90^\circ)$$
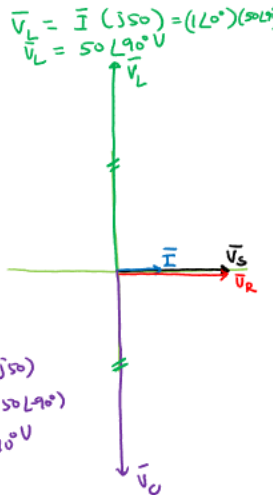
$$\bar{V}_C = 50 \angle -90^\circ \text{ V}$$



Phasor Diagram: Parallel RC

20

Assume $\bar{V} = 1 \angle 0^\circ \text{ V}$

calculate \bar{I}_R , \bar{I}_C , \bar{I}_S

$$50 \mu\text{F} \rightarrow \frac{-j}{(2000 \times 50 \times 10^{-6})}$$

$$= -j10$$




$$\bar{I}_R = \frac{\bar{V}}{5} = \frac{1 \angle 0^\circ}{5} = 0.2 \angle 0^\circ \text{ A}$$

$$\bar{I}_C = \frac{\bar{V}}{-j10} = \frac{1 \angle 0^\circ}{10 \angle -90^\circ} = 0.1 \angle 90^\circ \text{ A}$$

KCL @ node x

$$\bar{I}_S = \bar{I}_R + \bar{I}_C = (0.2 + j0.1)$$

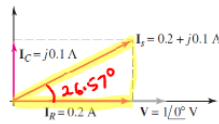
$$\bar{I}_S = 0.224 \angle 26.57^\circ \text{ A}$$



20

AC Circuits – Problem Solving

Determine $v(t)$ and $i(t)$

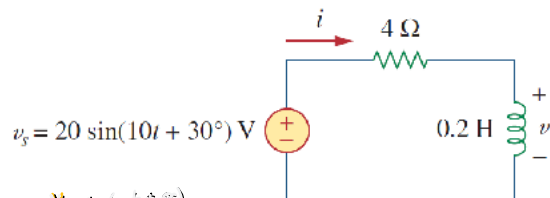

$$0.2 \text{ H} \Rightarrow j(10)(0.2) = j2 \Omega$$

$$0.2 \text{ H} \Rightarrow j(10)(0.2) = j2 \Omega$$

$$V_m \sin(\omega t + \phi)$$

$$20 \cos(10t + 30^\circ - 90^\circ) \Rightarrow 20 \cos(10t - 60^\circ)$$

$$\vec{V}_s = 20 \angle -60^\circ$$

$$\bar{Z}_R = 4 \Omega \angle 0^\circ$$

$$\bar{Z}_T = (4 + j2) \Omega$$

$$i(t) = \frac{20 \angle -60^\circ \text{ V}}{(4 + j2) \Omega} = 2.45 \angle -86.57^\circ$$

$$i(t) = 2.45 \cos(10t - 86.57^\circ)$$