

B

Bachelor of Engineering – Mechatronics Program

Programmable Logic Controllers: MENG 3500 Course

Quiz No. 3 [5 marks]

Time allocated: 20 minutes


If you need more space for each question, please use the back of the sheet.

Student Name: Michael McCorkell

Student Number: N01500049


0,9 / 5

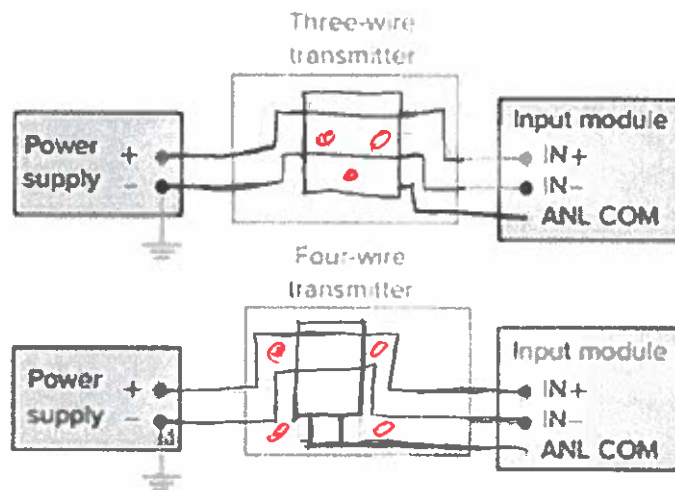1. Wire three -and four – sensor/transmitters into an analog module. [0.5 mark]




0,2

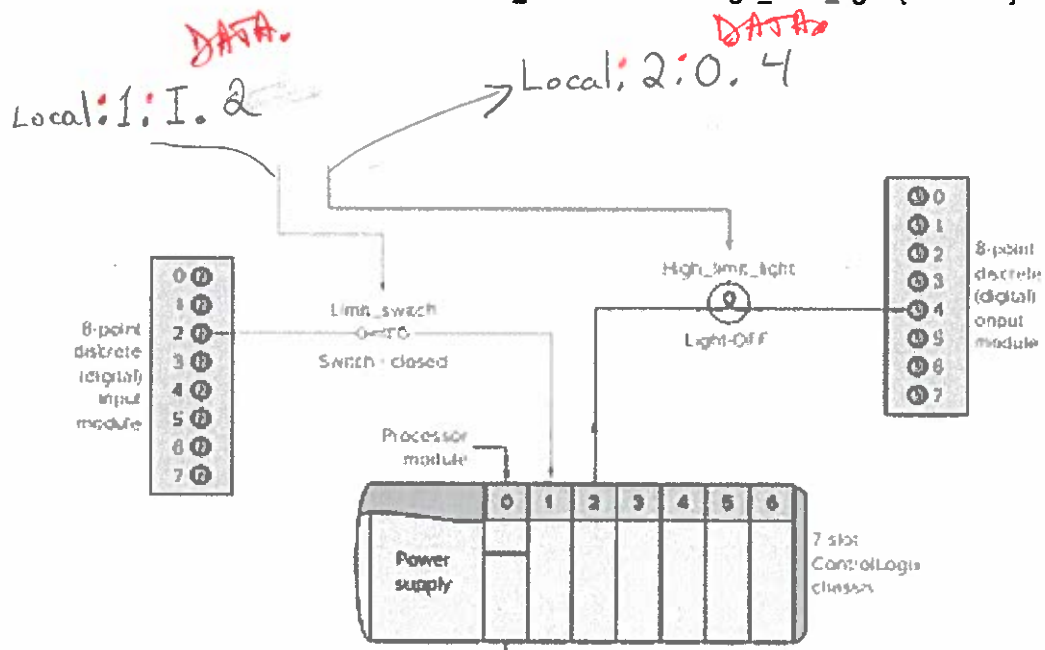2. Provide the addresses for the Limit_switch and the High_limit_light [0.5 mark]




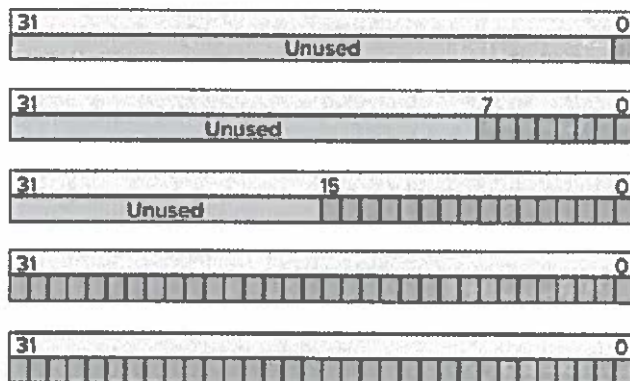3. Name the types of base tag data [0.5 mark]




4. Wire the four types of analog input transmitters [1 marks]

1769-IF4X0F2 Mixed Transmitter Inputs

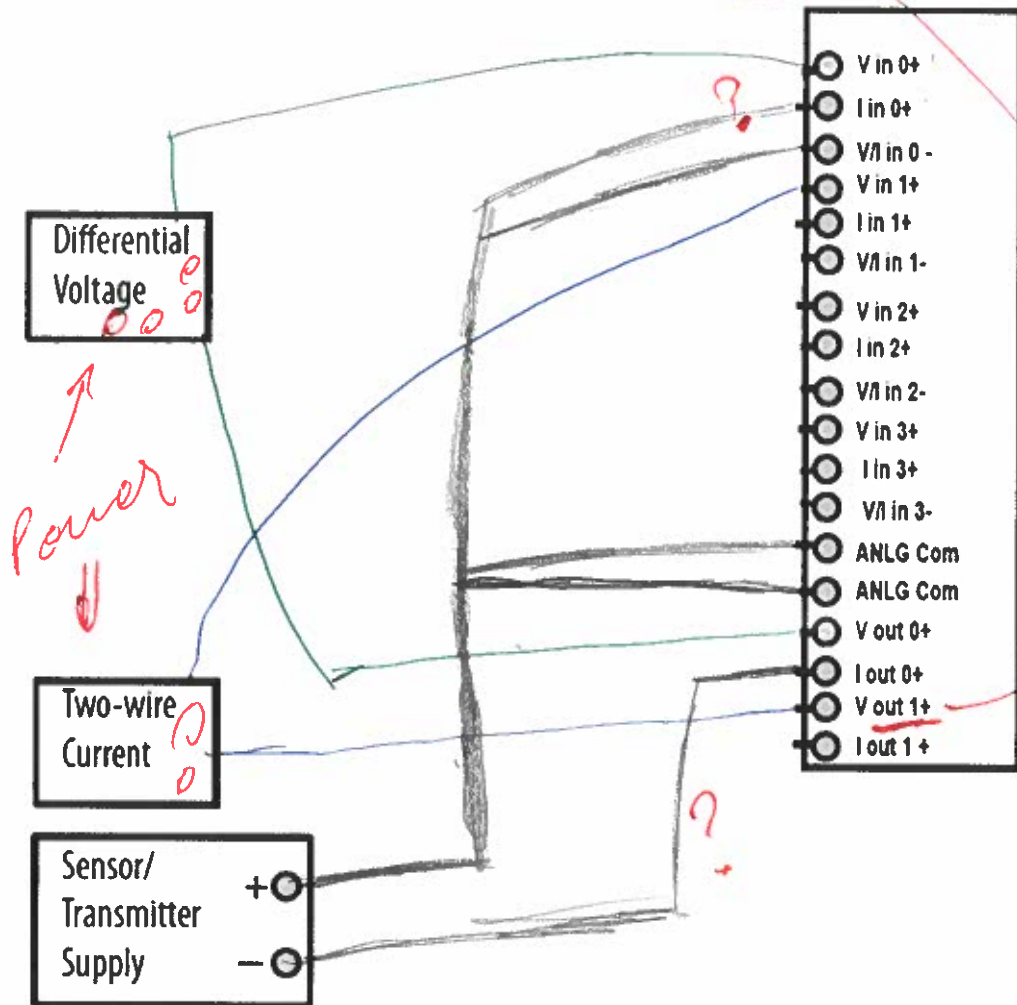

5. Wire the analog output transducer [0.5 marks]

1769-IF4XOF2 Outputs

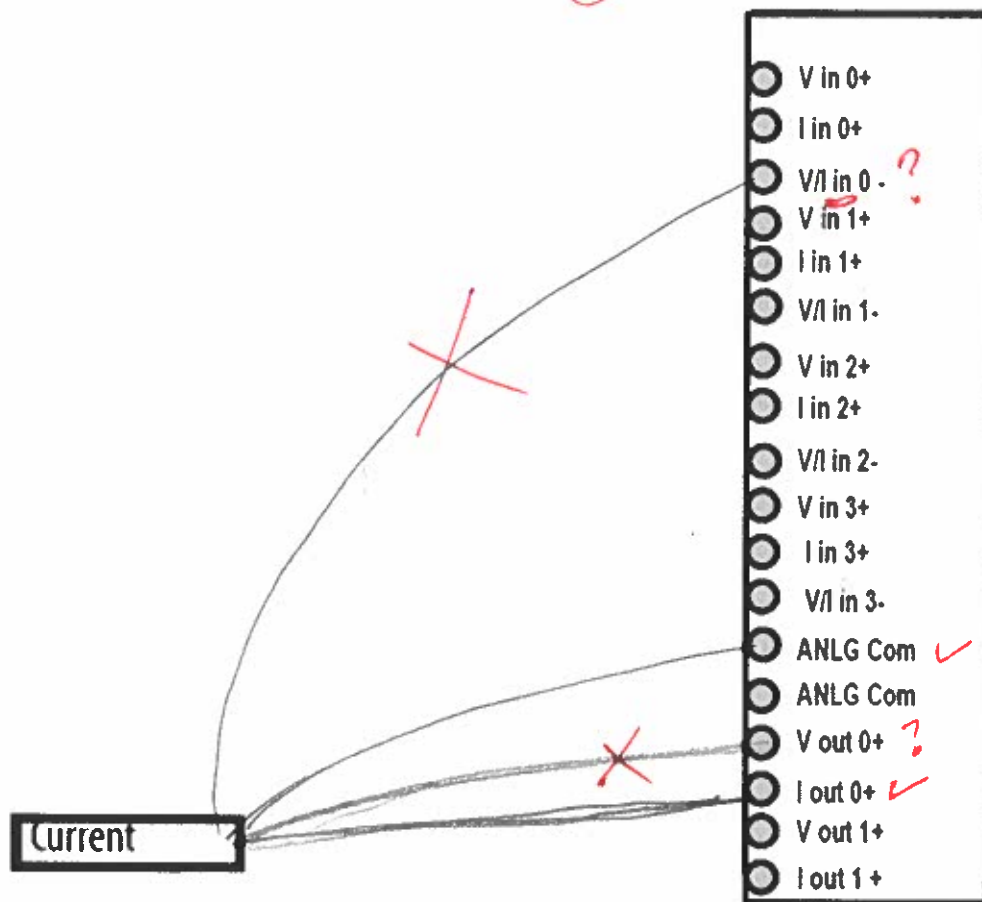

6. A temperature transmitter provides a voltage signal in the range from 1 – 5 VDC for changes in temperature from 100° C – 200° C. The voltage signal is connected to an analog module PLC that has the specifications below (Bit 0 – Bit 6 are always 0, not used). Calculate the Temperature in engineering units. The requirements are for you to find a formula that will correlate the temperature in degrees Celsius with the digits received from the analog input module. [2 marks]

Full Module Range
0.0 to +10.5V dc

10.5 V – 32640 PLC UNITS


$$100^{\circ}\text{C} = 4\text{VDC}$$

BIT 15	BIT 14	BIT 13	BIT 12	BIT 11	BIT 10	BIT 9	BIT 8	BIT 7	BIT 6	BIT 5	BIT 4	BIT 3	BIT 2	BIT 1	BIT 0
SIGN	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

DECIMAL 0

BIT 15	BIT 14	BIT 13	BIT 12	BIT 11	BIT 10	BIT 9	BIT 8	BIT 7	BIT 6	BIT 5	BIT 4	BIT 3	BIT 2	BIT 1	BIT 0
SIGN	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0

DECIMAL 32640

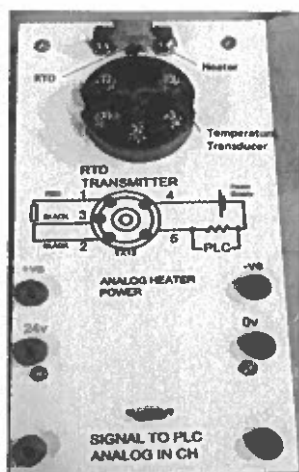

$$100^{\circ}\text{C} = 4\text{VDC}$$